

## Series and Parallel Circuits

ECE 2100 Circuit Analysis Laboratory  
updated 6 September 2016

### Equipment and Supplies

variable DC voltage source
digital multimeter (2)
resistors (1/4W)
1 k $\Omega$
2.2 k $\Omega$
2.7 k $\Omega$
4.7 k $\Omega$
one random value
one rheostat

### Pre-Laboratory Assignment

1. Consider the following series circuit. Derive a formula to calculate voltage  $V_1$  in terms of  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ , and  $V_S$ . Repeat for  $V_2$ ,  $V_3$ , and  $V_4$ .


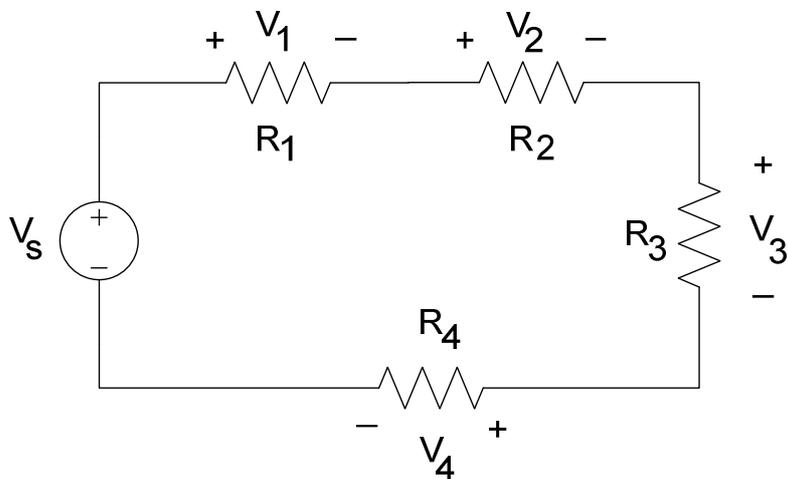



Figure 1. Series Circuit with Four Resistors

2. For the following circuit, derive a formula for  $R_2$  in terms of  $R_1$ ,  $V_2$ , and  $V_S$ .

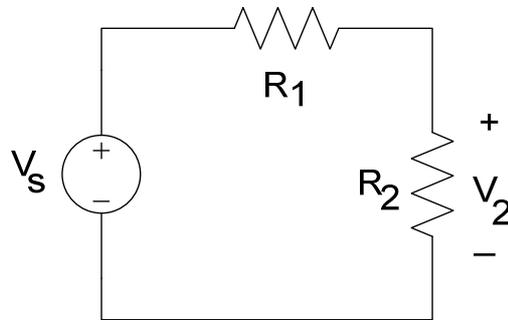

**Figure 2. Series Circuit with Two Resistors**

3. Consider the following combination series/parallel circuit. Note that each of the nodes is numbered 0 (reference node or “ground”), 1, or 2.

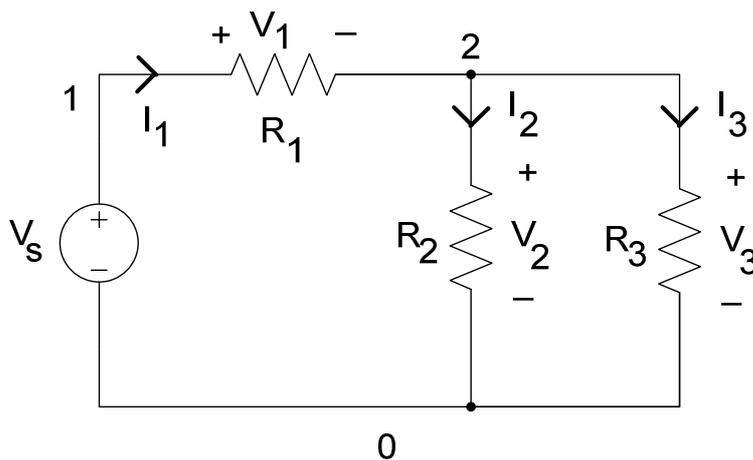

**Figure 3. Combination Series/Parallel Circuit**

- Derive a formula for the total resistance  $R_T$  “seen by”  $V_S$  in terms of  $R_1$ ,  $R_2$ , and  $R_3$ .
- Derive a formula for the current  $I_1$  in terms of  $R_1$ ,  $R_2$ ,  $R_3$ , and  $V_S$ .
- Use the *current divider rule* to find a formula for  $I_2$  in terms of  $I_1$ ,  $R_2$ , and  $R_3$ .
- Use the *current divider rule* to find a formula for  $I_3$  in terms of  $I_1$ ,  $R_2$ , and  $R_3$ .

## Procedures

### Part One

1. Consider the following resistor values for the circuit of Figure 1:

$R_1$	1000 $\Omega$ (1k $\Omega$ )
$R_2$	2200 $\Omega$ (2.2k $\Omega$ )
$R_3$	2700 $\Omega$ (2.7k $\Omega$ )
$R_4$	4700 $\Omega$ (4.7k $\Omega$ )

**Table 1. Resistor Values for Part One**

Complete a table with the nominal (column Nominal R) and actual (column Measured R) resistor values. Using the formulas derived in your pre-lab and the measured resistances (column Measured R), calculate the predicted voltages (column Calculated V) assuming a source voltage of  $V_S=5V$ .

2. Using the resistor values provided in Table 1, construct the circuit shown in Figure 1. Have your instructor check your work before energizing the circuit.
3. Energize your circuit and measure the voltages across each resistor. Record your findings, along with the voltages computed in step 1 (column Calculated V) in a table formatted as indicated. Compute the error percentage between the computed and experimental voltages.

	Nominal R	Measured R	Calculated V (using measured resistances)	Measured V	V % Error
$R_1, V_1$					
$R_2, V_2$					
$R_3, V_3$					
$R_4, V_4$					

### Part Two

4. Select a nominal 4.7k $\Omega$  resistor as  $R_1$ . Carefully measure the value of this resistance. Select a second resistor from the resistor "grab bag" as  $R_2$ . Using resistors  $R_1$  and  $R_2$ , assemble the circuit of Figure 2.
5. Measure the voltage  $V_2$  across resistor  $R_2$ . From this, along with the equation derived in the pre-lab, calculate the theoretical resistance  $R_2$ . How do the theoretical and actual values

compare?

**Part 3**

6. Measure the values of three resistors with nominal values as indicated in Table 2.

R <sub>1</sub>	2.2kΩ
R <sub>2</sub>	2.7kΩ
R <sub>3</sub>	4.7kΩ


**Table 2. Resistor Values for Part 3**

- Using the resistor values of Table 2 assemble the circuit of Figure 3 without the voltage source. Measure and record the total resistance R<sub>T</sub> “seen by” V<sub>S</sub>. Compare to the value of R<sub>T</sub> computed for the actual resistor values using the equation derived in the pre-lab.
- Now connect a V<sub>S</sub>=5V voltage source (initially OFF of course).
- Calculate the currents I<sub>1</sub>, I<sub>2</sub> and I<sub>3</sub> using your equation from the pre-lab. Tabulate your results.
- After your instructor checks your circuit, energize the circuit with V<sub>S</sub>=5V. Now measure the voltage drops across and currents through each resistor with polarities as indicated in Figure 3. Tabulate and calculate the current percent errors.

	Resistance R		Calculated I		Measured V		% Error Current
	Nominal	Measured	Calculated (using measured resistances)	Measured	Calculated (using measured resistances)	Measured	
R <sub>1</sub>							
R <sub>2</sub>							
R <sub>3</sub>							

**Part 4**

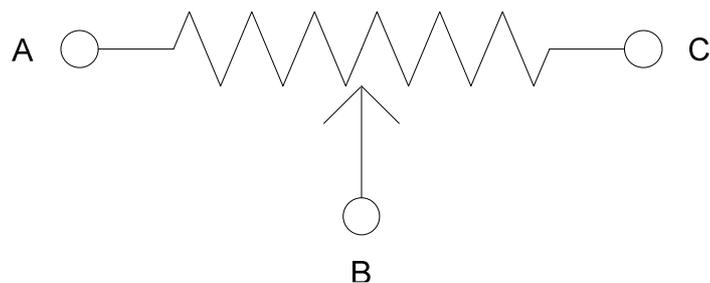
11. A symbol for a *rheostat* or *variable resistor* is shown below.



A rheostat works by varying the position of the “wiper” connected to terminal B. This position is often moved by turning a shaft. Notice that as the wiper position changes, the resistance from A to B and from B to C also changes, while the resistance from A to C remains the same. The resistances  $R_{AB}$  and  $R_{BC}$  can vary from 0 to  $R_{AC}$  and are related by the equation

$$\frac{R_{AB}}{R_{AC}} + \frac{R_{BC}}{R_{AC}} = 1.$$

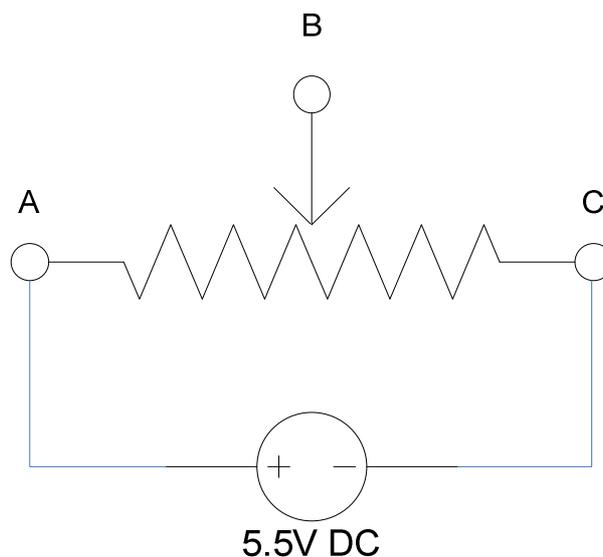12. Obtain a rotating arm rheostat. Observe and measure the resistance between the terminals A-C and B-C as the shaft is rotated.
13. Assemble the following circuit assuming a resistance ratio of 50%. Measure and record the voltages across A-C and B-C. Be sure to indicate the assumed polarity of measured voltages in your lab notebook.



14. Set the wiper to make the voltage drop across terminals B-C of the rheostat to be 1.5 V (label your assumed voltage polarity). Calculate what resistance between terminals B-C is required to obtain the 1.5V drop. Verify your answer by disassembling your circuit and measuring the resistance directly.

### Analysis

Begin by reviewing the guidelines for keeping your lab notebook. Perform this analysis work in your lab notebook.

1. Be sure to calculate and comment on all percent errors computed in this lab (in appropriate sections of your notebook).

2. Does the data of **Part 1** satisfy Kirchhoff's voltage law? Explain.
3. Does the data of **Part 3** satisfy Kirchhoff's current law? Explain
4. Show from the data of **Part 4** that the rheostat functions as a voltage divider.

### **Credits and Copyright**

Adapted from material developed by current and former ECE faculty, including Professor Joseph Kelemen. Thanks to Sepehr Emamian and Dr. Randall Fisher for improvements to this lab.

© 2016 Damon A. Miller and Frank L. Severance. All rights reserved.