

# ECE 2100

## Circuit Analysis

### Lesson 14

### Chapter 4: Circuit Theorems

### Thevenin's Theorem

**Daniel M. Litynski, Ph.D.**

**<http://homepages.wmich.edu/~dlitynsk/>**



# Circuit Theorems - Chapter 4

4.1 Motivation

4.2 Linearity Property

4.3 Superposition

4.4 Source Transformation

4.5 Thevenin's Theorem

4.6 Norton's Theorem

4.7 Maximum Power Transfer

# ECE 2100


## Circuit Analysis

### Lesson 13

#### Chapter 4: Circuit Theorems

#### Superposition Principle

#### Source Transformations



# ECE 2100

## Circuit Analysis

### Lesson 14

### Chapter 4: Circuit Theorems

### Thevenin's Theorem

**Daniel M. Litynski, Ph.D.**


**<http://homepages.wmich.edu/~dlitynsk/>**

# 4.5 Thevenin's Theorem (1)


It states that a linear two-terminal circuit (Fig. a) can be replaced by an equivalent circuit (Fig. b) consisting of a voltage source  $V_{TH}$  in series with a resistor  $R_{TH}$ ,

where

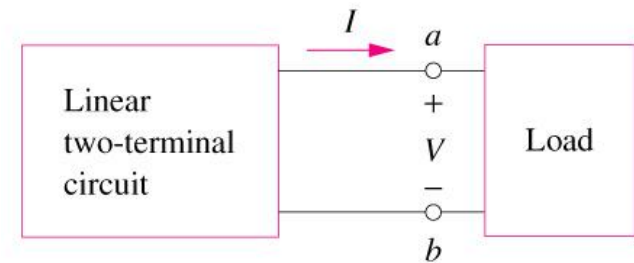- $V_{TH}$  is the open-circuit voltage at the terminals.
- $R_{TH}$  is the input or equivalent resistance at the terminals when the independent sources are turned off.



(a)



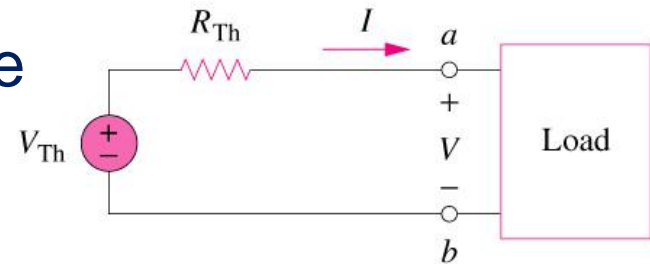


(b)

# 4.5 Thevenin's Theorem (2)
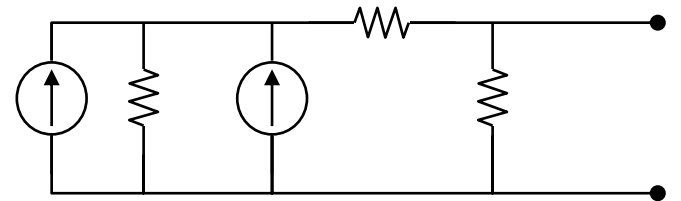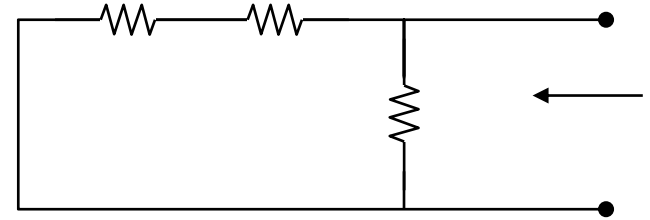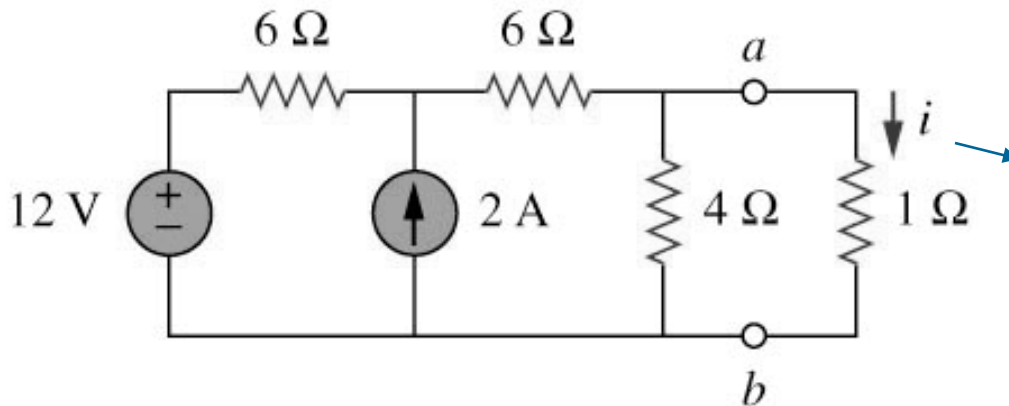
## Example 5

Using Thevenin's theorem, find the equivalent circuit to the left of the terminals in the circuit shown below. Hence find  $i$ .






\*Refer to in-class illustration, textbook, answer  $V_{TH} = 6V$ ,  $R_{TH} = 3\Omega$ ,  $i = 1.5A$


# 4.5 Thevenin's Theorem (3)
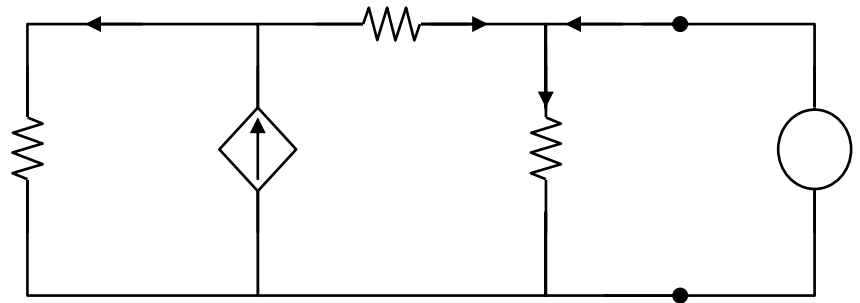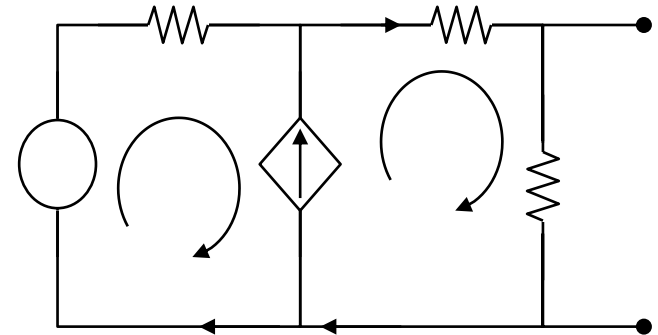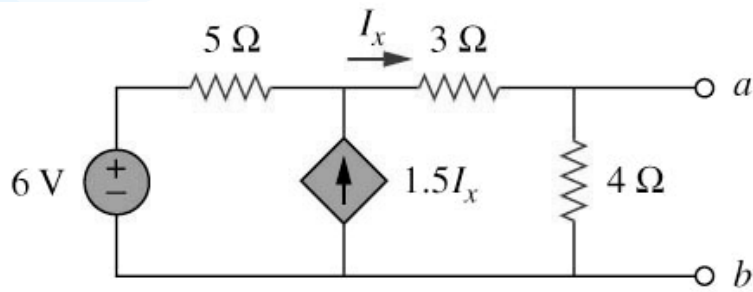
## Example 6


Find the Thevenin equivalent circuit of the circuit shown below to the left of the terminals.



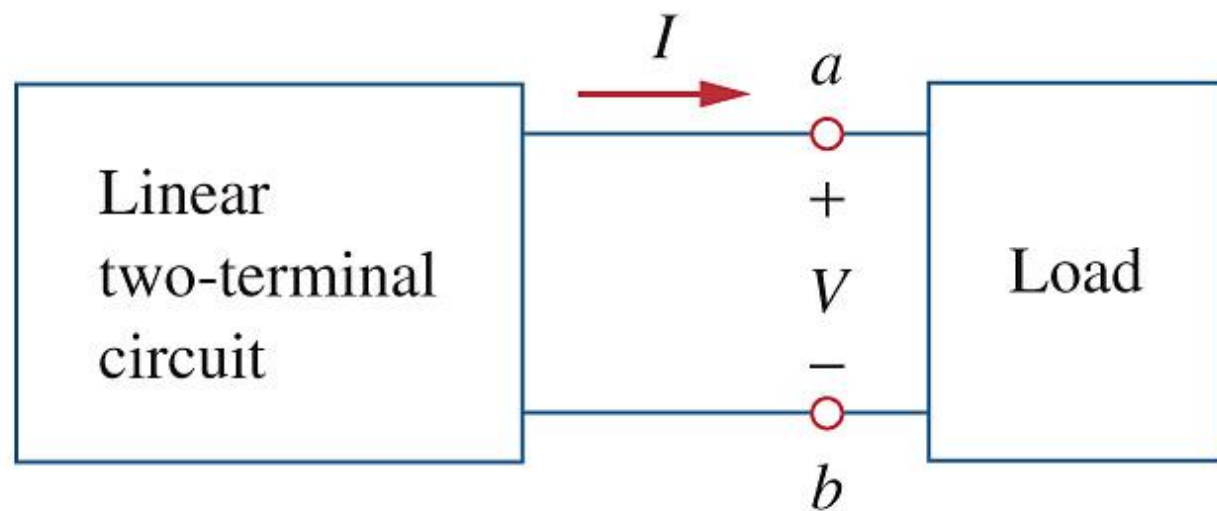
\*Refer to in-class illustration, textbook, answer  $V_{TH} = 5.33V$ ,  $R_{TH} = 3\Omega$




(a)

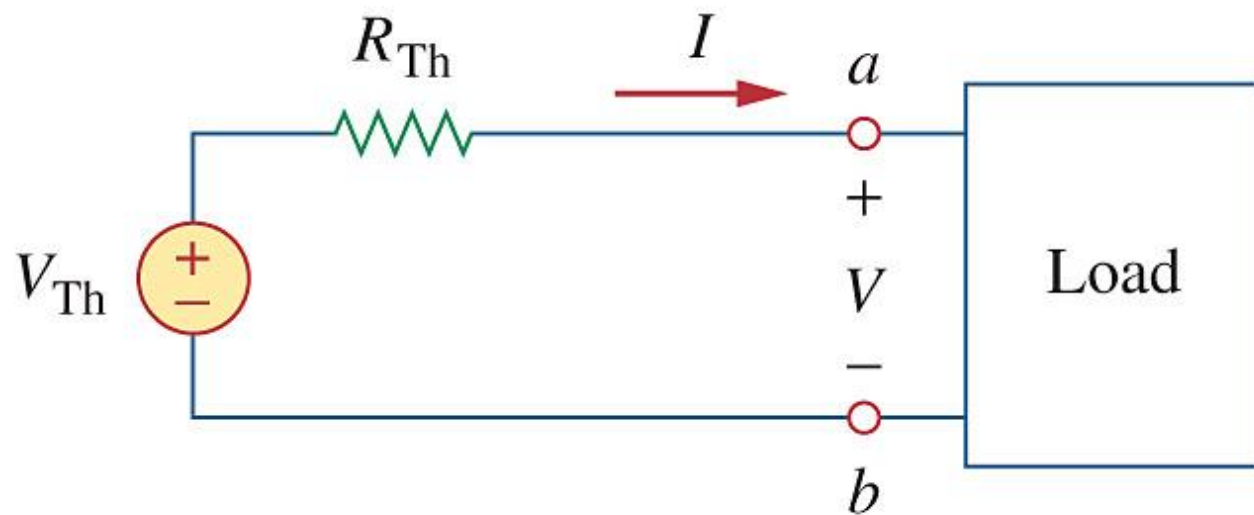

(b)




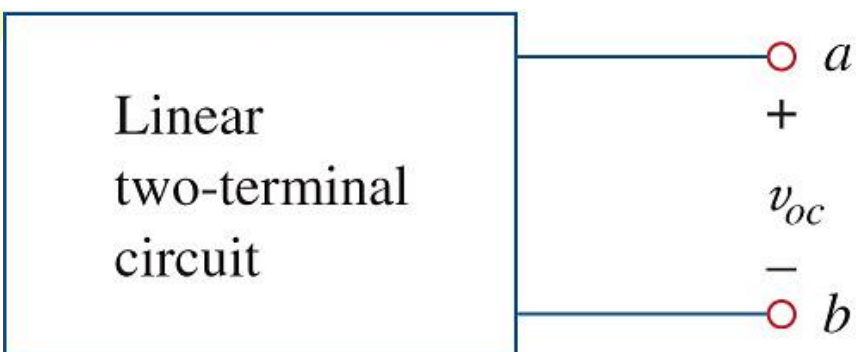Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$V_{Th} = v_{oc}$$


(a)

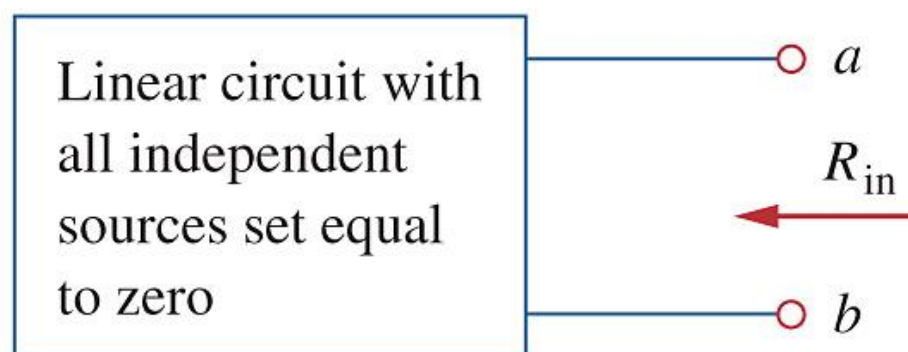

$$R_{Th} = R_{in}$$


(b)



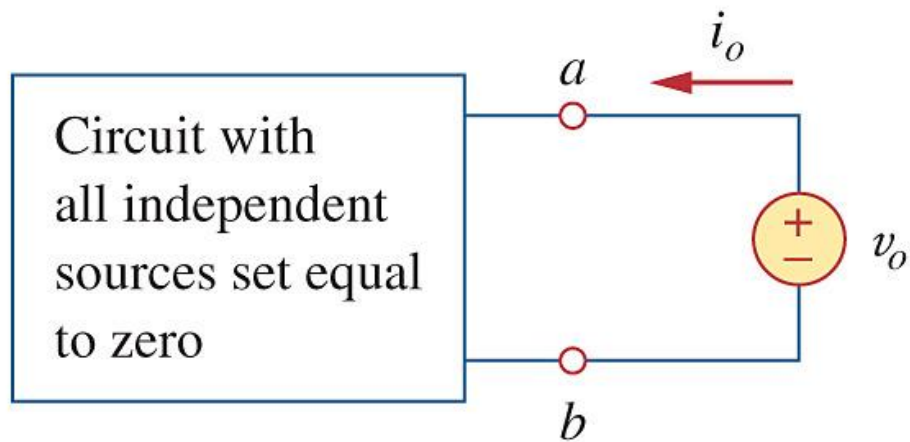


$$R_{Th} = \frac{v_o}{i_o}$$

(a)

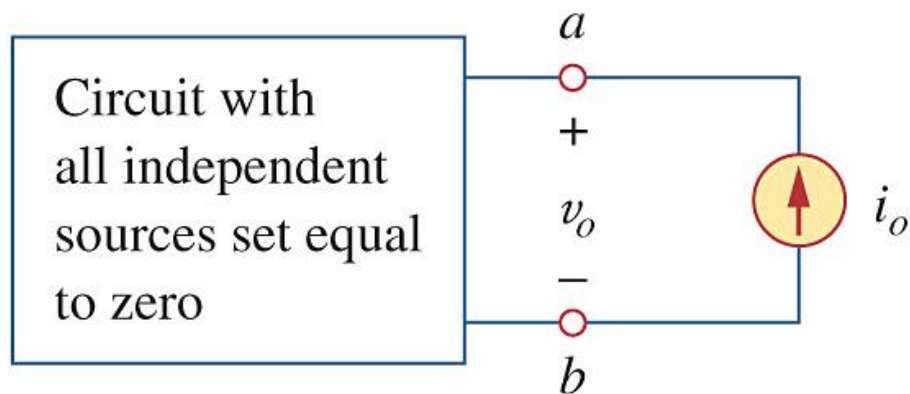


$$R_{Th} = \frac{v_o}{i_o}$$

(b)

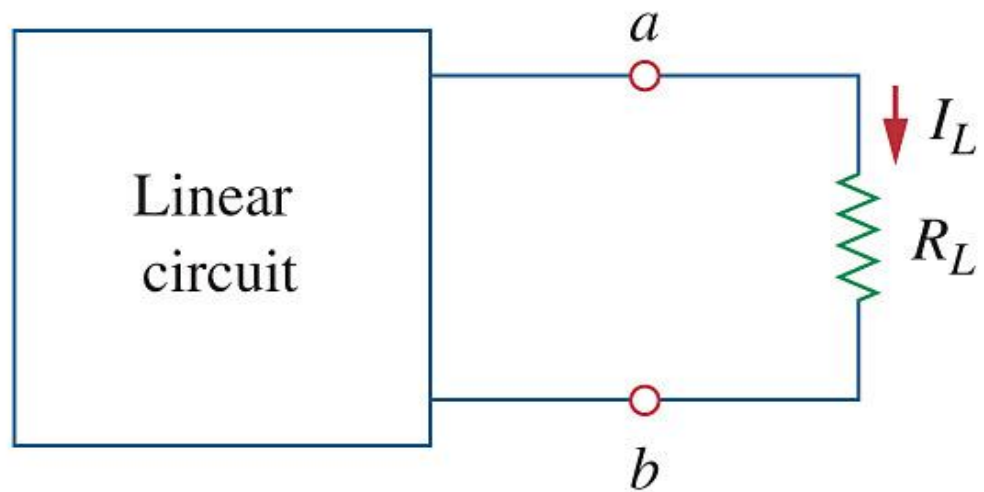


(a)

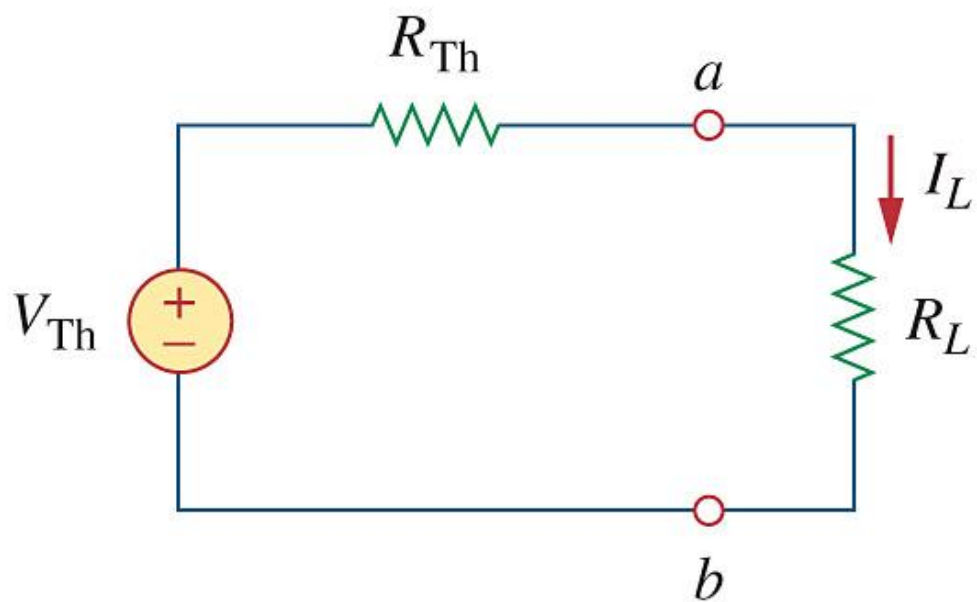


(b)

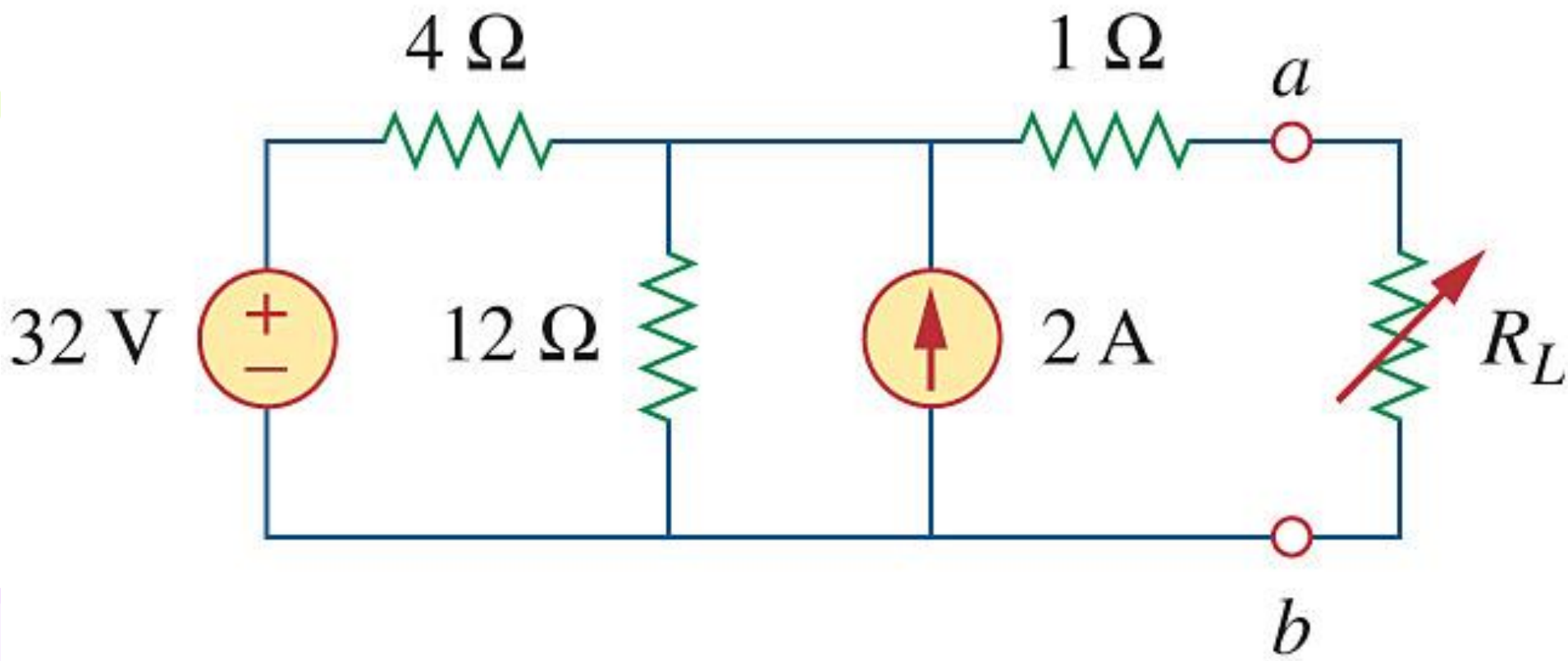
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



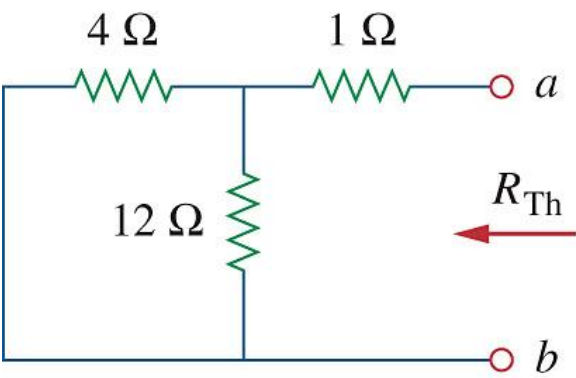Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




(a)

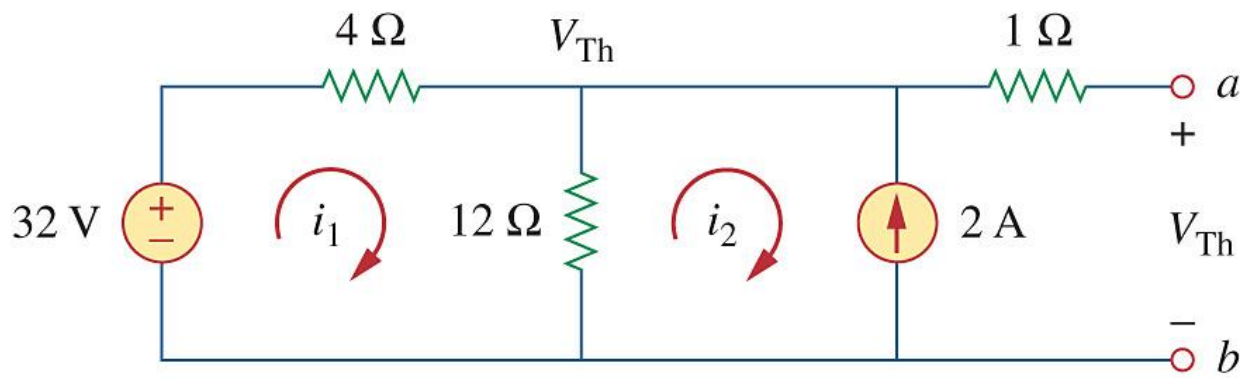



(b)

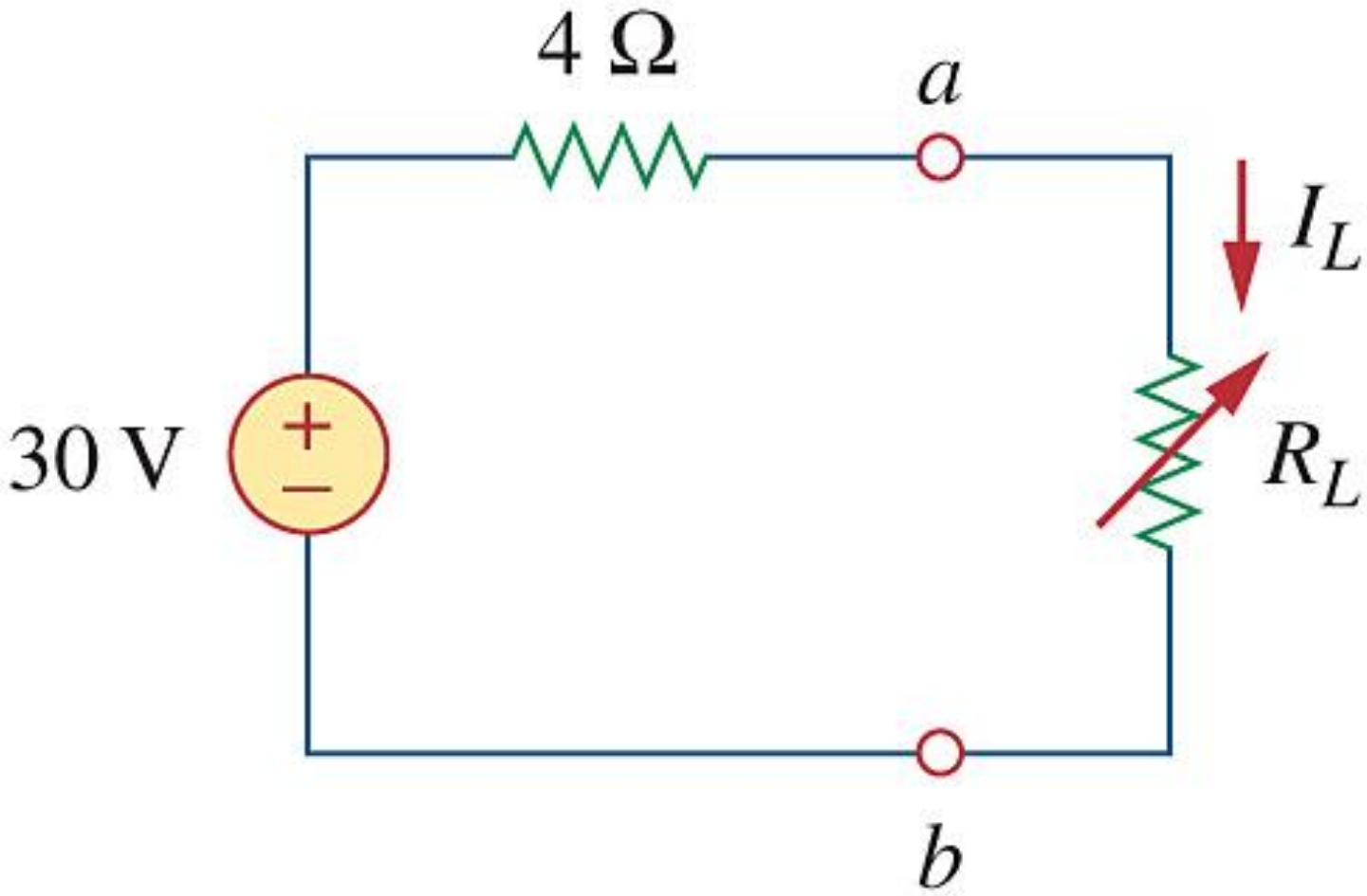Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




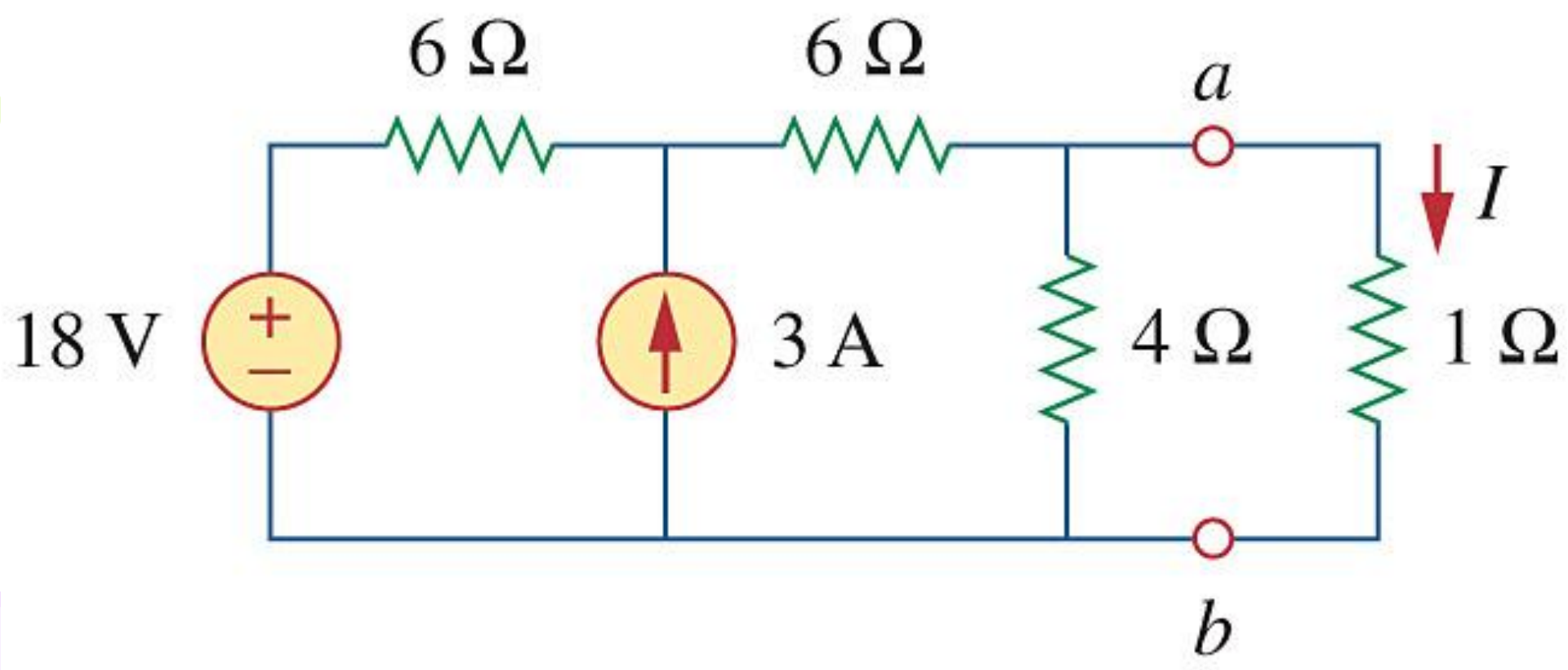Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




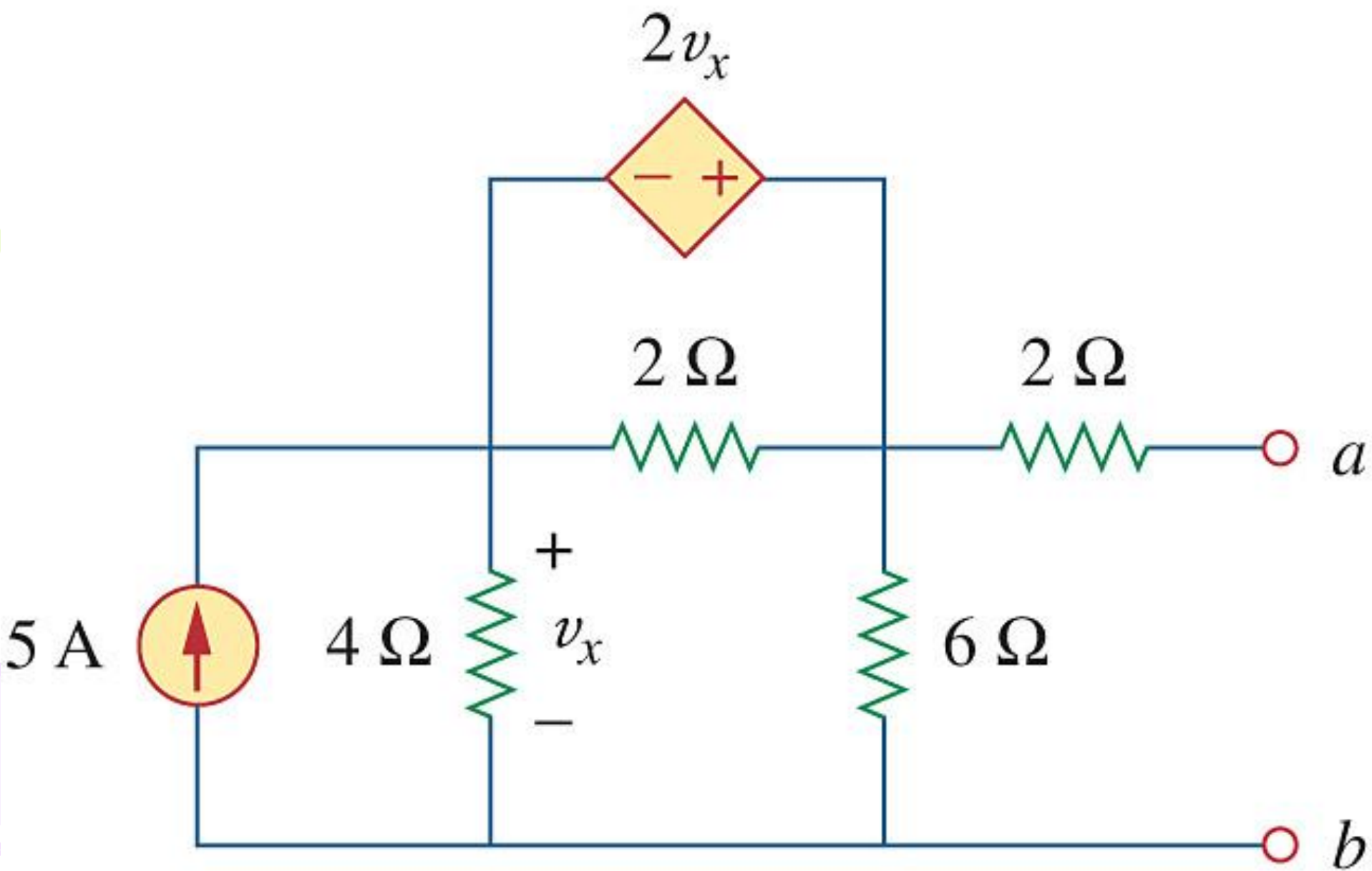

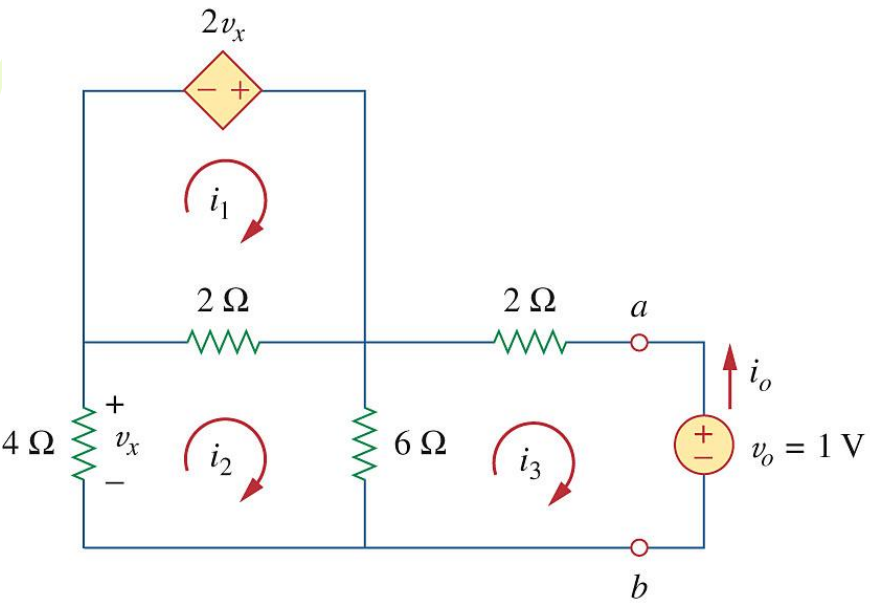Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




(a)

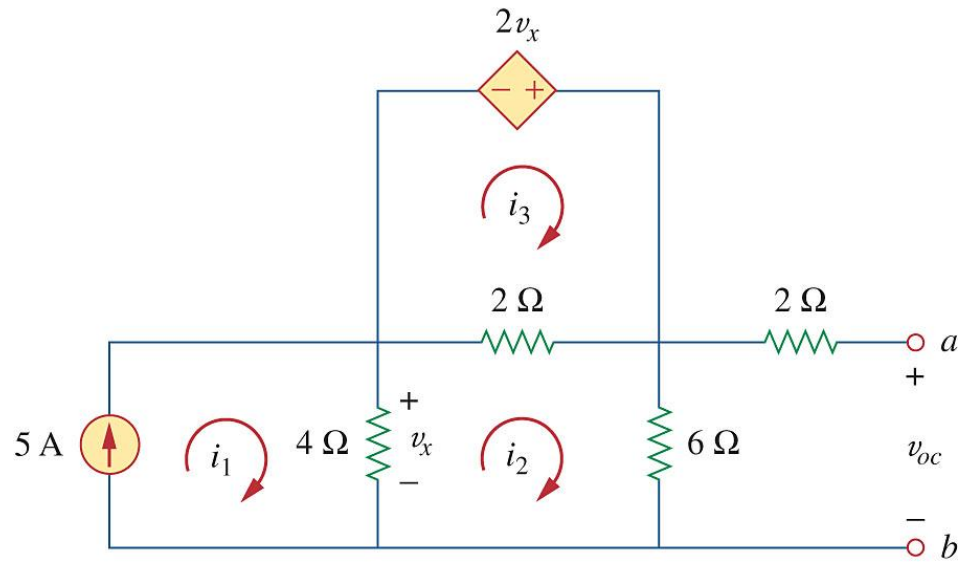



(b)

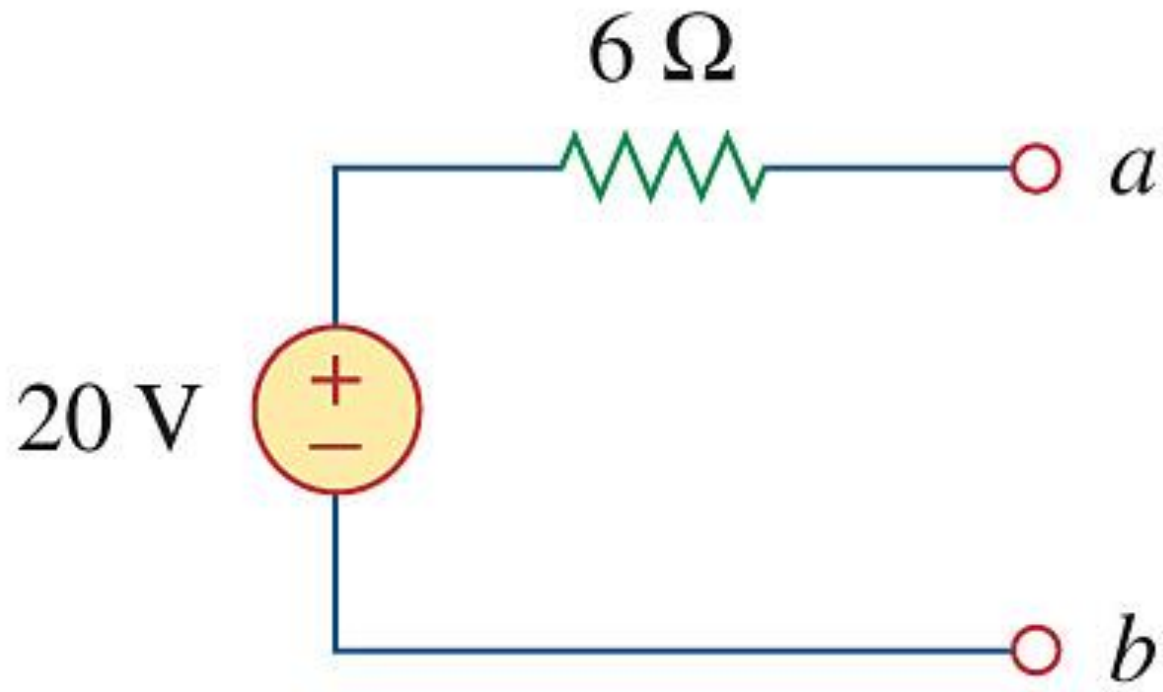Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




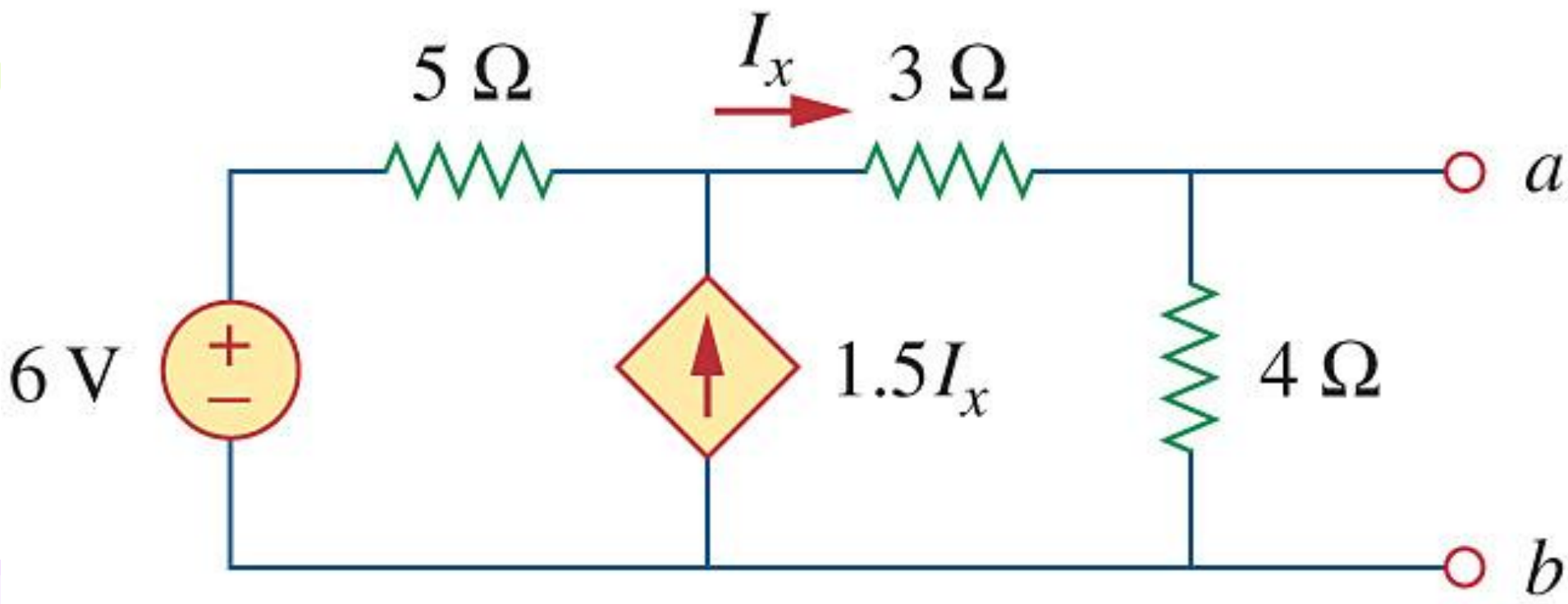Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




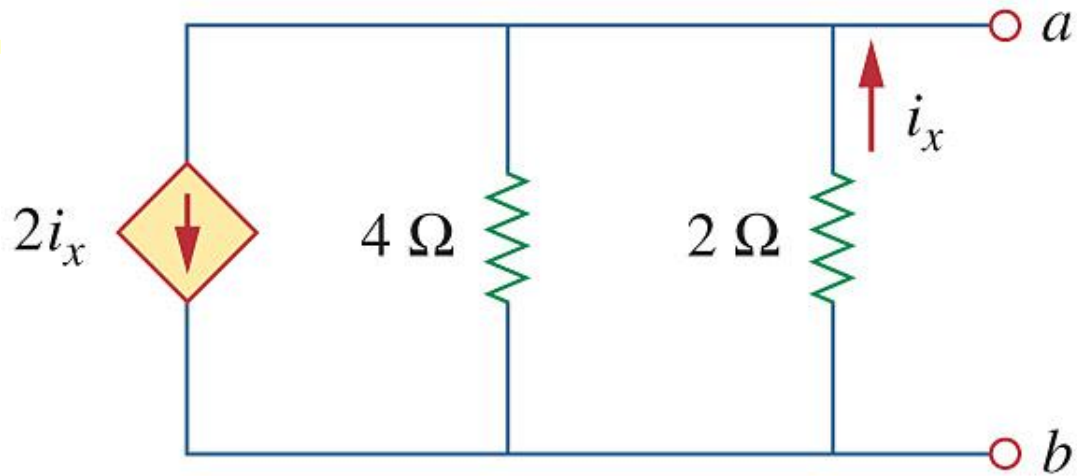


(a)

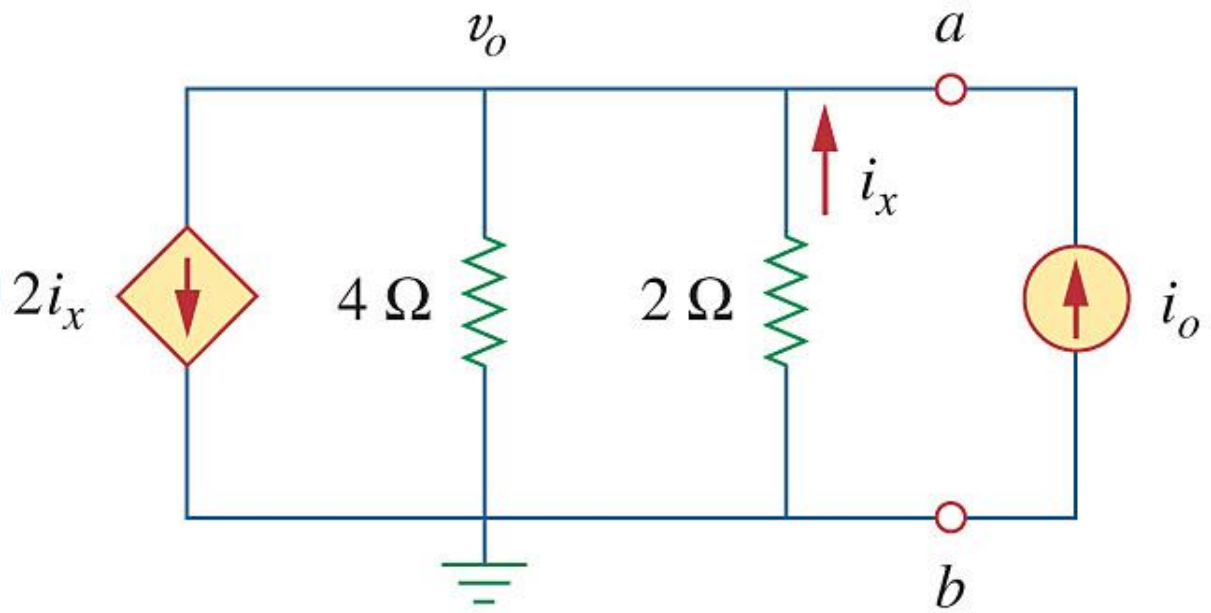

(b)

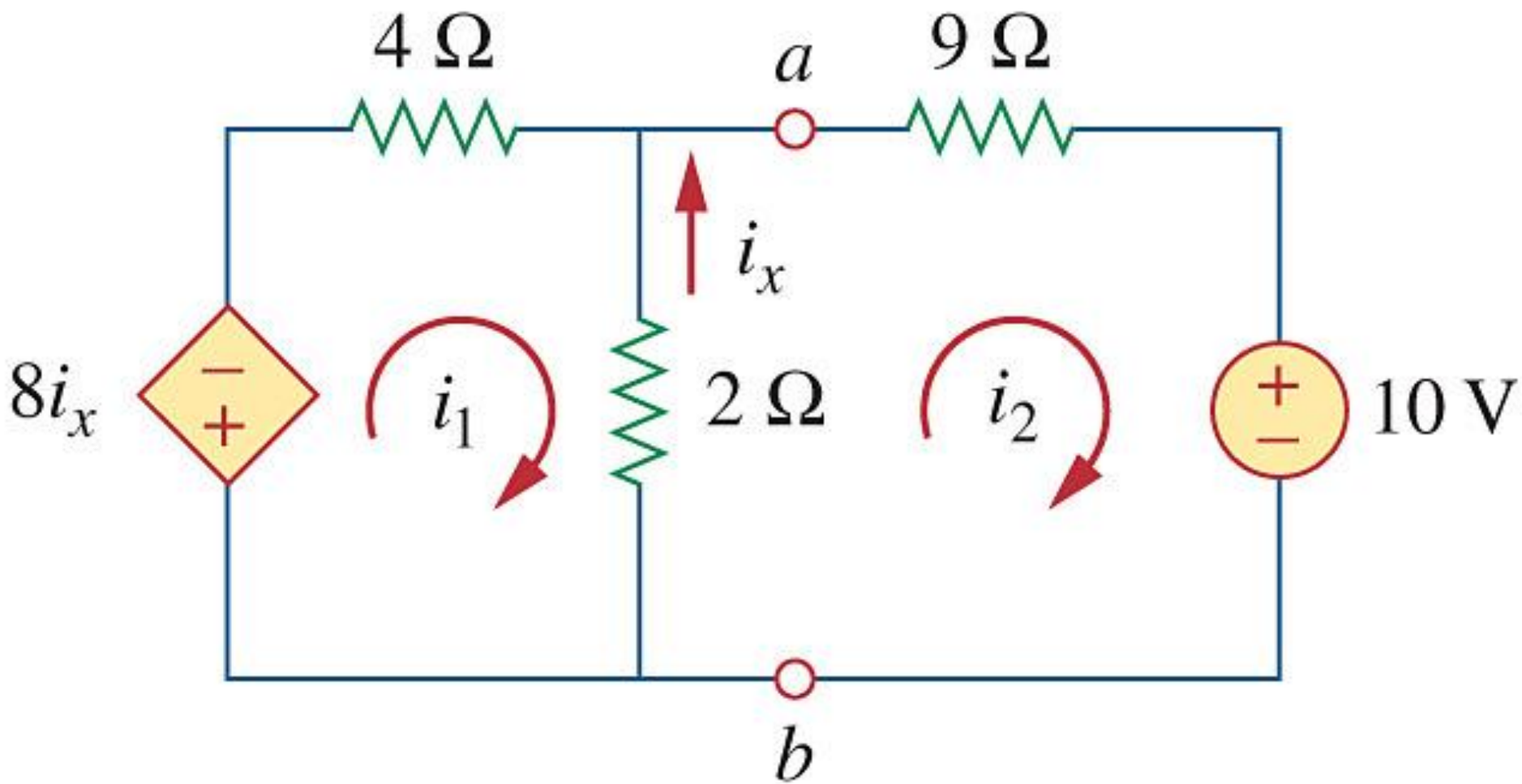

(c)

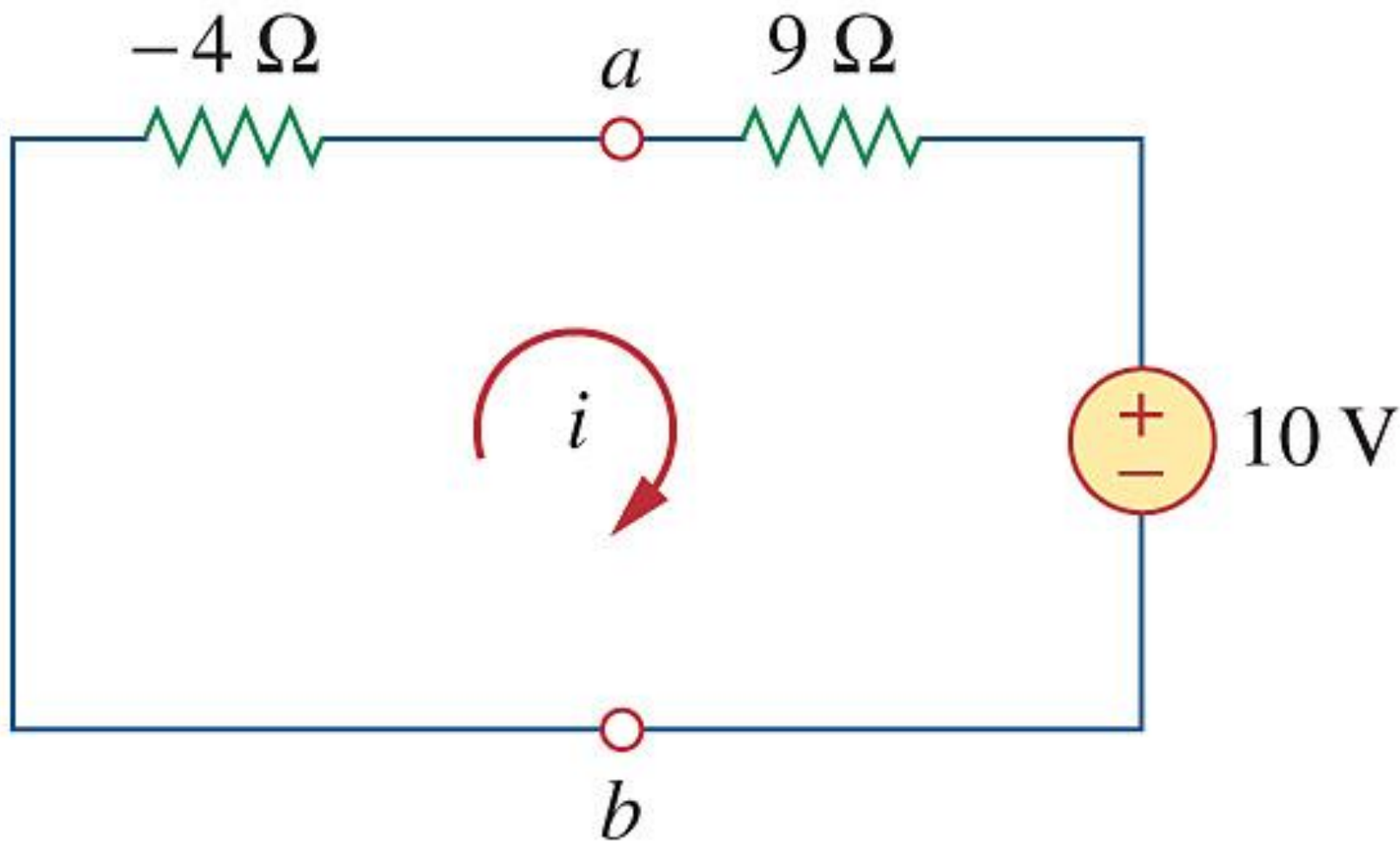

(d)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

