

# ECE 2100

## Circuit Analysis

Lesson 15  
Chapter 4: Circuit Theorems  
Norton's Theorem  
Maximum Power Transfer  
Wheatstone Bridge  
Operational Amplifiers

**Daniel M. Litynski, Ph.D.**

**<http://homepages.wmich.edu/~dlitynsk/>**



# Circuit Theorems - Chapter 4

4.1 Motivation

4.2 Linearity Property


4.3 Superposition

4.4 Source Transformation

4.5 Thevenin's Theorem

4.6 Norton's Theorem

4.7 Maximum Power Transfer



# ECE 2100

## Circuit Analysis


### Lesson 14

### Chapter 4: Circuit Theorems

### Thevenin's Theorem

**Daniel M. Litynski, Ph.D.**

**<http://homepages.wmich.edu/~dlitynsk/>**



# ECE 2100

## Circuit Analysis

Lesson 15

Chapter 4: Circuit Theorems

Norton's Theorem

Maximum Power Transfer

Wheatstone Bridge

Operational Amplifiers

# 4.6 Norton's Theorem (1)


It states that a linear two-terminal circuit can be replaced by an equivalent circuit of a current source  $I_N$  in parallel with a resistor  $R_N$ , where

- $I_N$  is the short circuit current through the terminals.
- $R_N$  is the input or equivalent resistance at the terminals when the independent sources are turned off.


**The Thevenin's and Norton equivalent circuits are related by a source transformation.**

$$R_N = R_{Th}$$


$$I_N = V_{Th}/R_{Th}$$

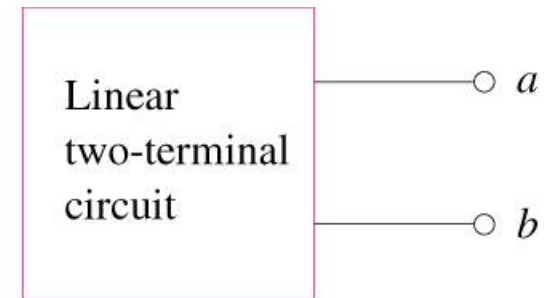


(a)

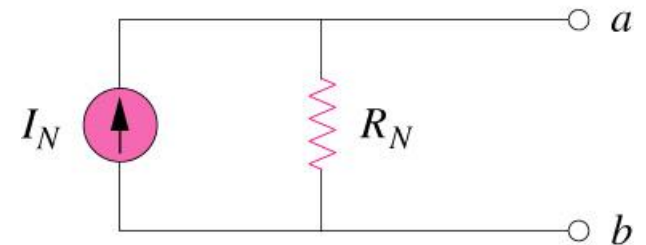


(b)

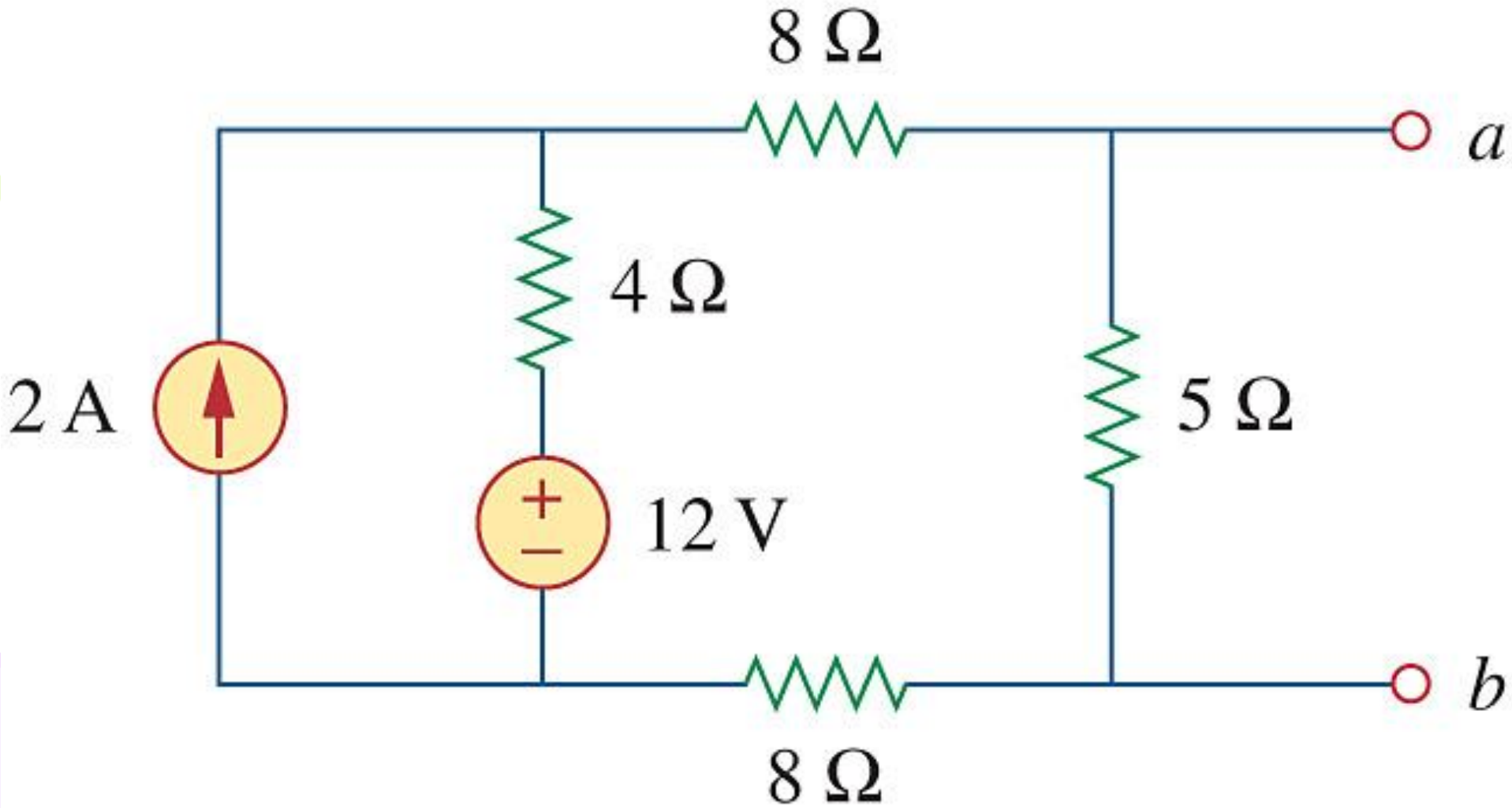


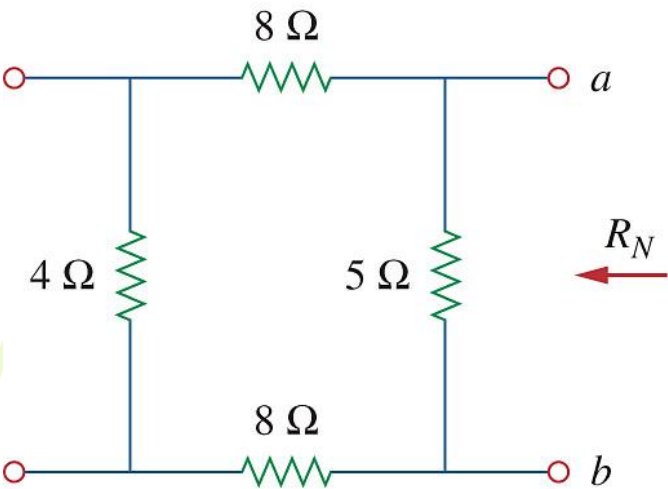

(a)

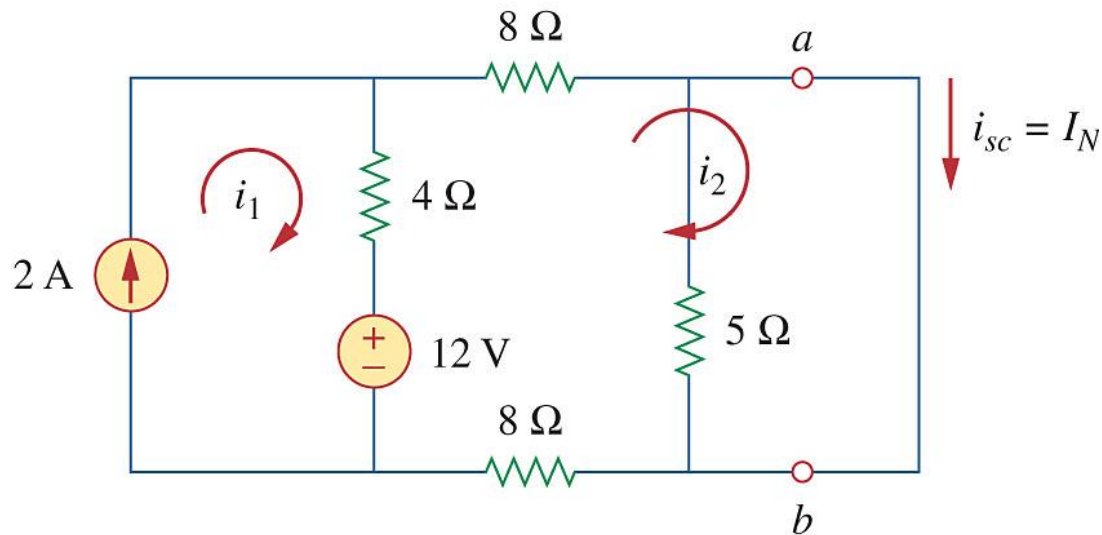



(b)

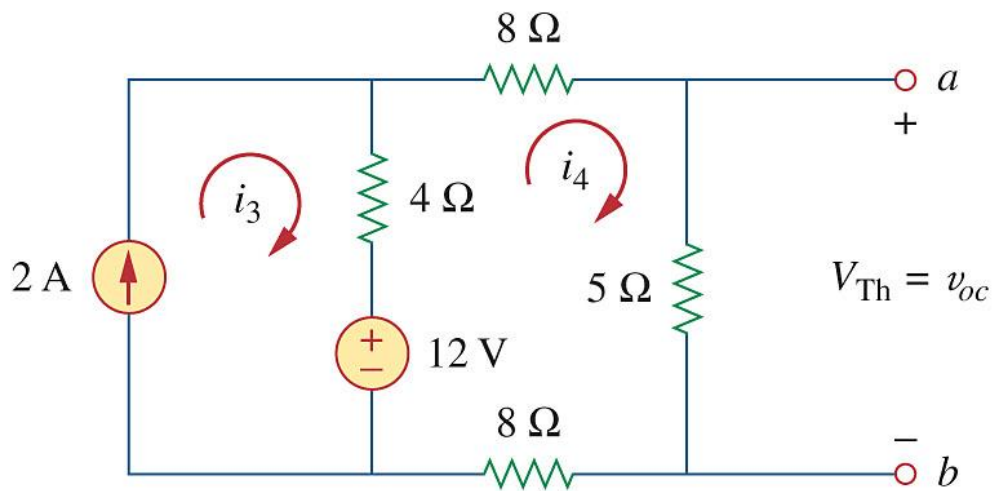


(c)

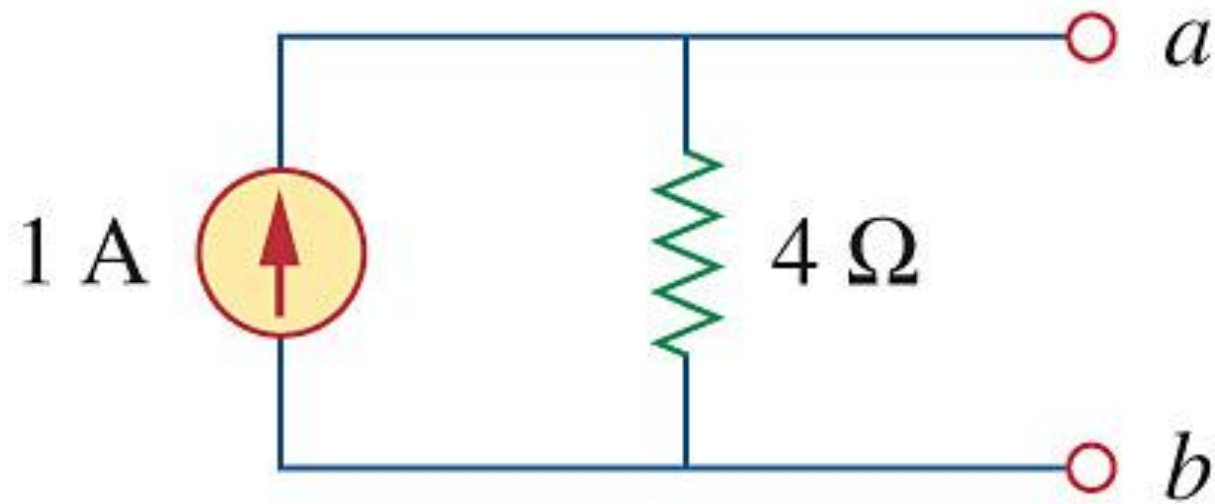Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




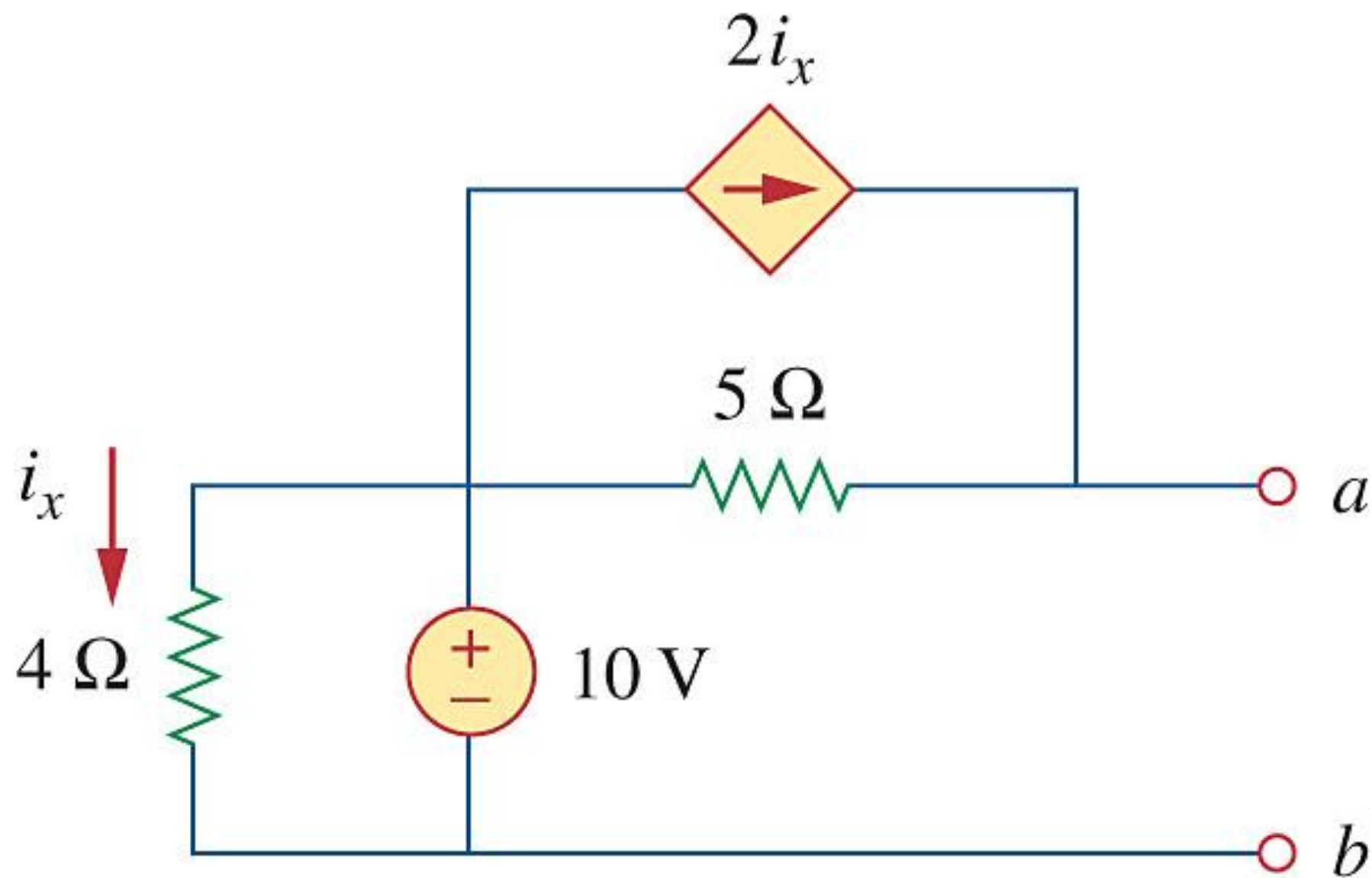

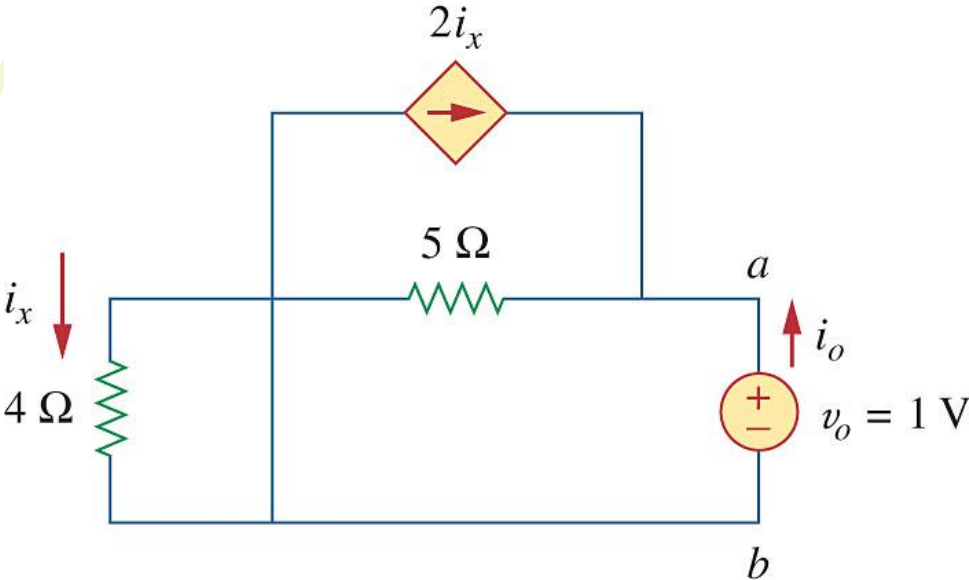Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




(a)

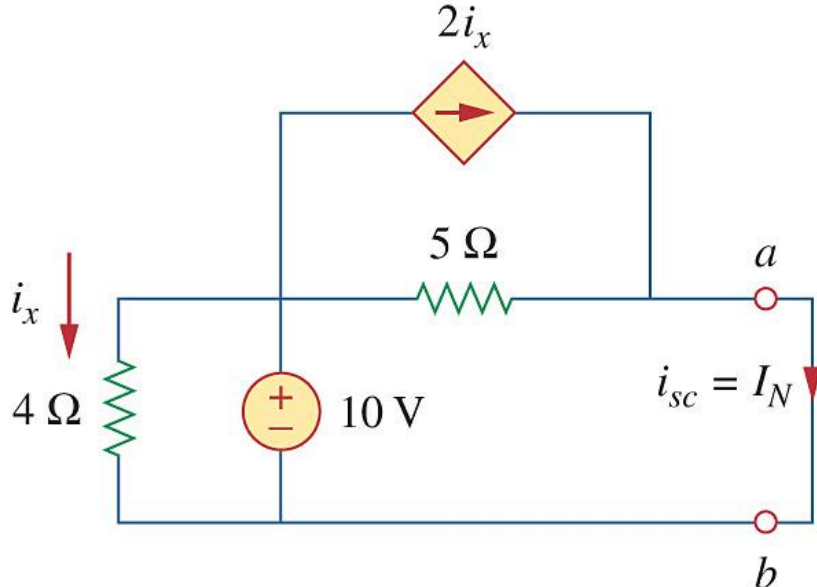

(b)



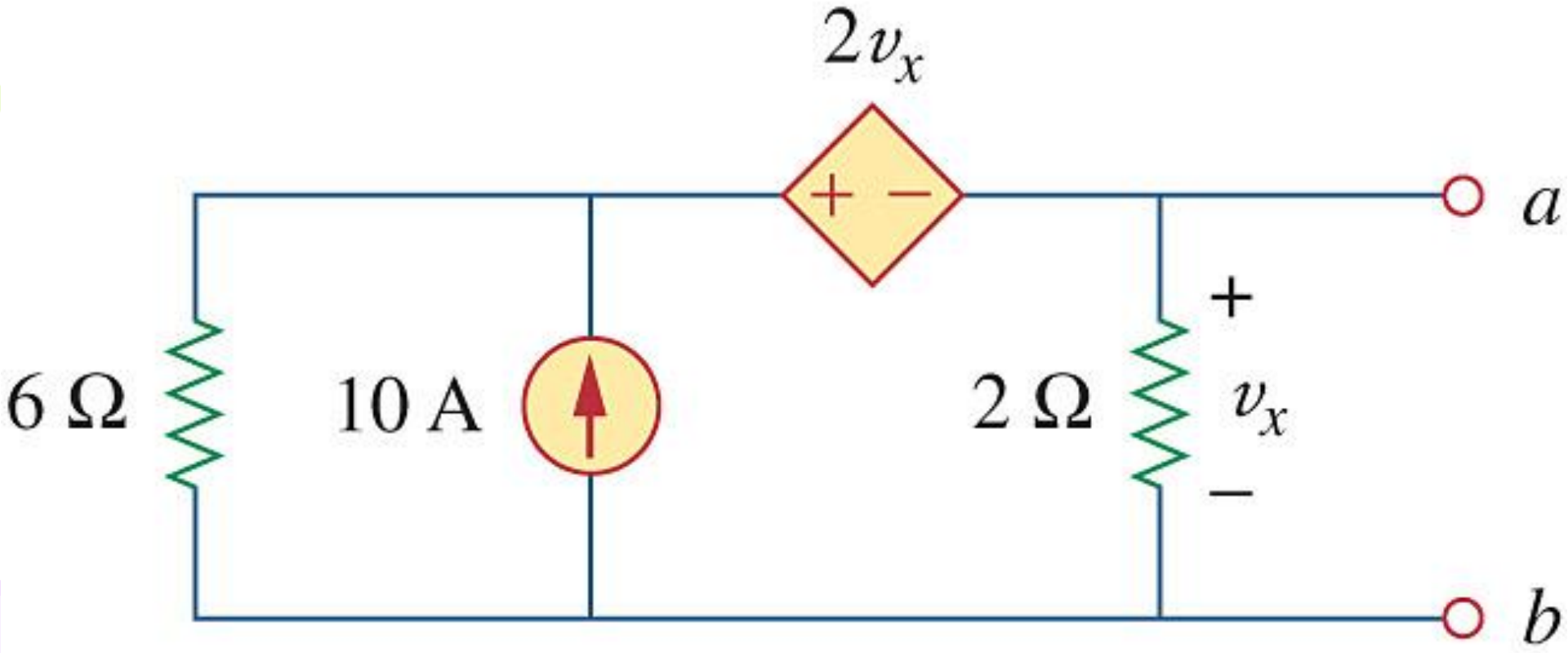
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



# 4.6 Norton's Theorem (2)
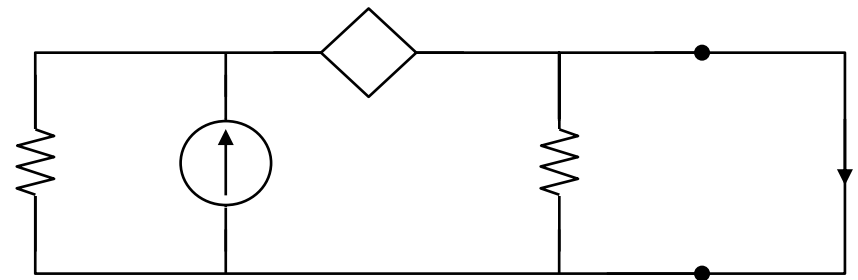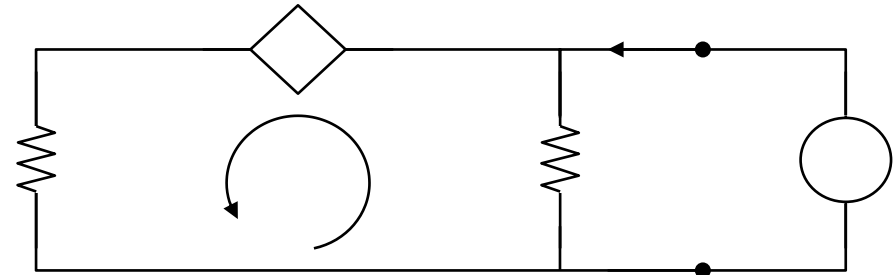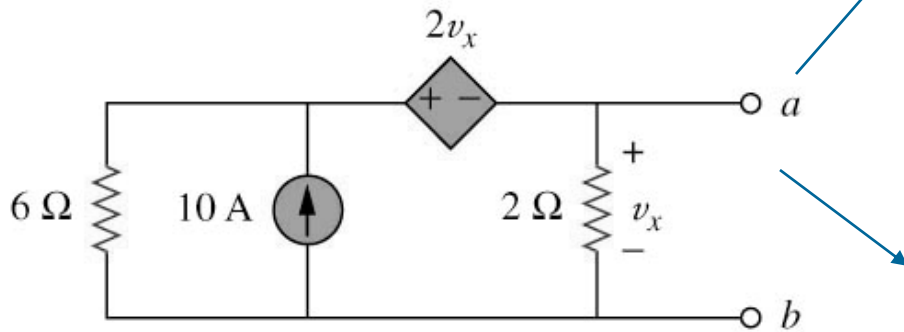
## Example 7

Find the Norton equivalent circuit of the circuit shown below.



\*Refer to in-class illustration, textbook,  $R_N = 1\ \Omega$ ,  $I_N = 10\ \text{A}$ .