


# ECE 2100

## Circuit Analysis

Lesson 22  
Chapter 6:  
Inductance 1, 2

**Daniel M. Litynski, Ph.D.**


**<http://homepages.wmich.edu/~dlitynsk/>**

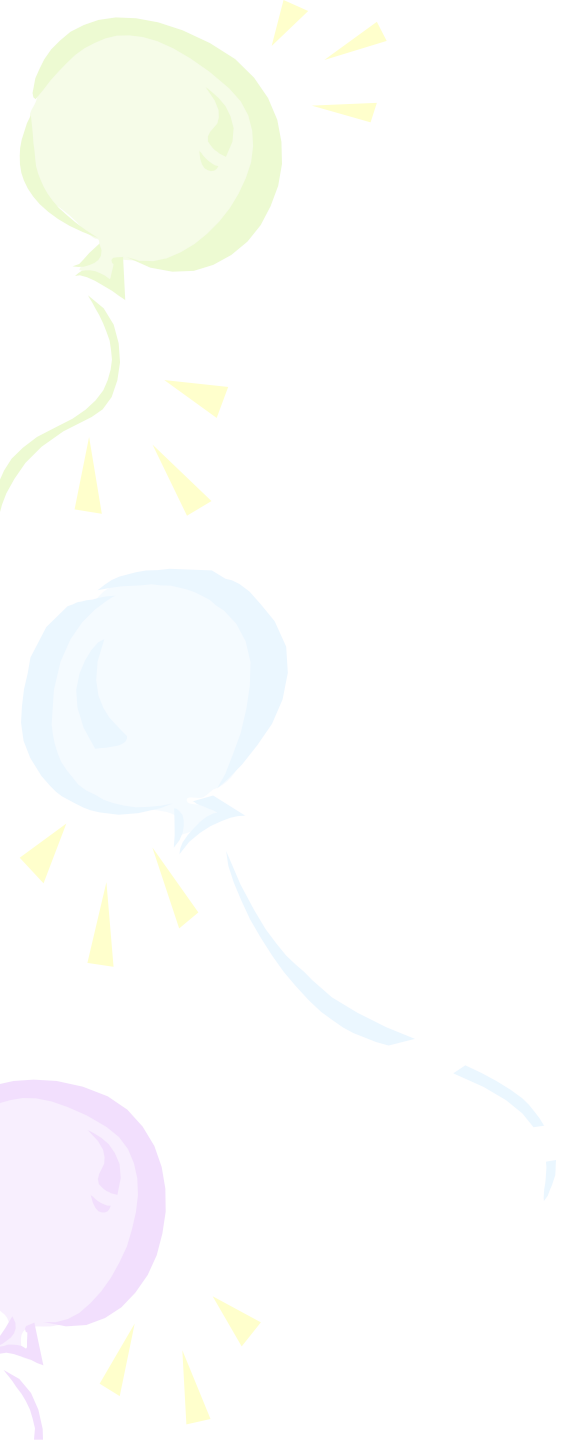A decorative graphic on the left side of the slide features three balloons: a green one at the top, a light blue one in the middle, and a purple one at the bottom. Each balloon is attached to a string and has several small yellow triangular shapes around it, resembling streamers or confetti.

# ECE 2100

## Circuit Analysis

Review  
Lesson 20  
Chapter 6:  
Capacitance

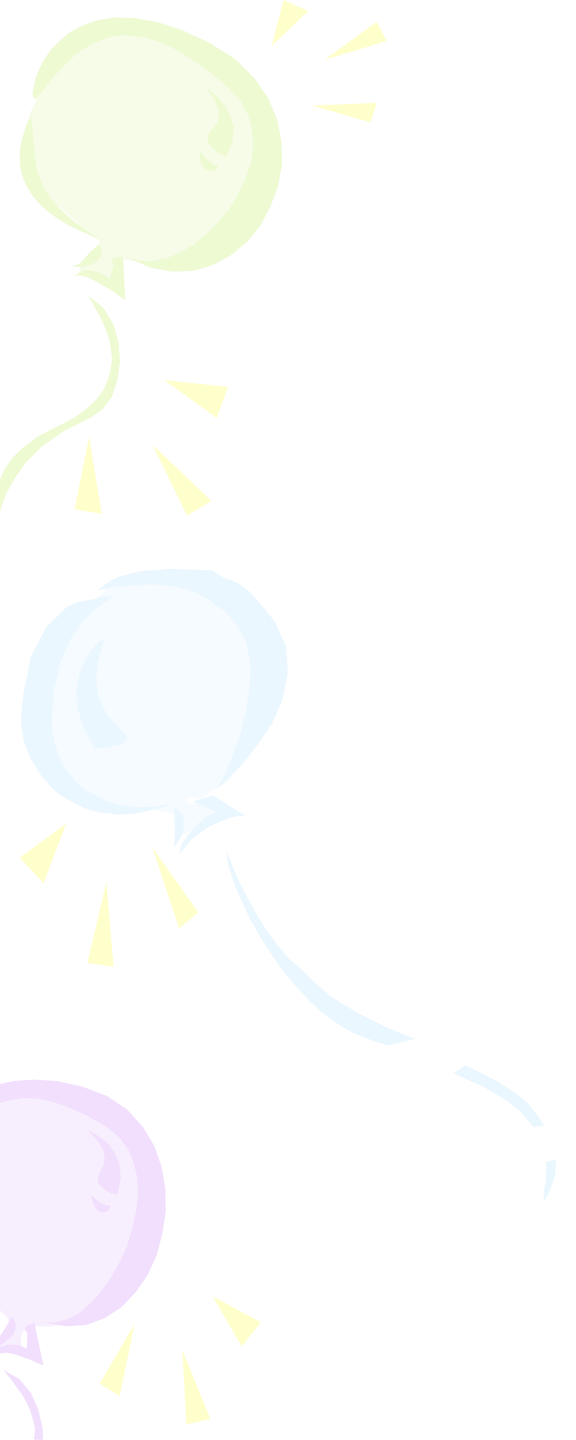A decorative graphic on the left side of the slide features three balloons: a green one at the top, a light blue one in the middle, and a purple one at the bottom. Each balloon is attached to a string and has several small yellow triangular shapes radiating from it, resembling streamers or confetti.


# ECE 2100

## Circuit Analysis

Lesson 22  
Chapter 6:  
Inductance 1, 2
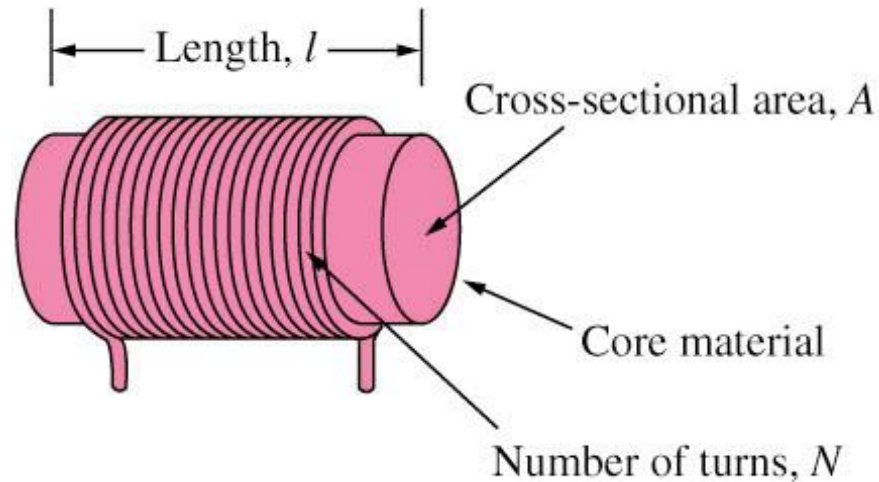
## 6.3 Inductors (1)


- An inductor is a passive element designed to store energy in its magnetic field.



- An inductor consists of a coil of conducting wire.




(a)

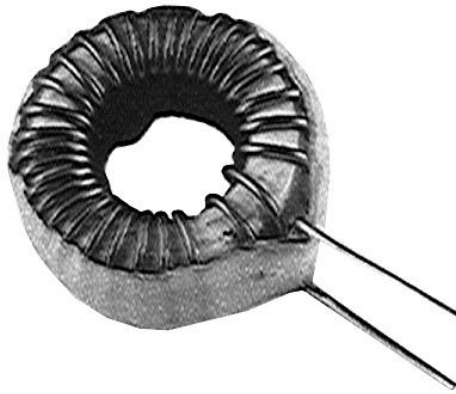


(b)




(c)

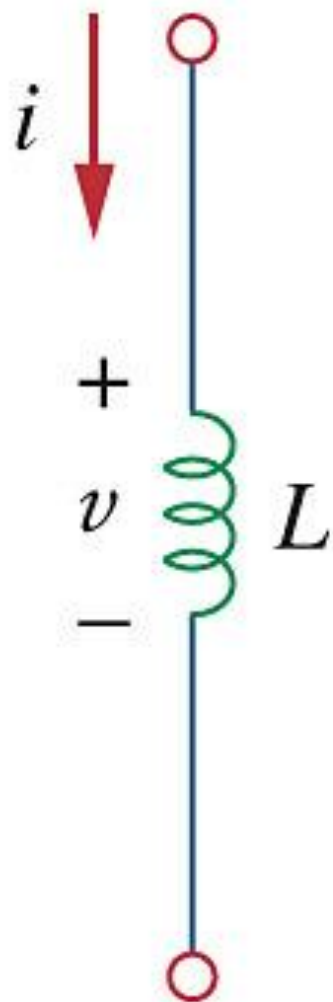

(a)

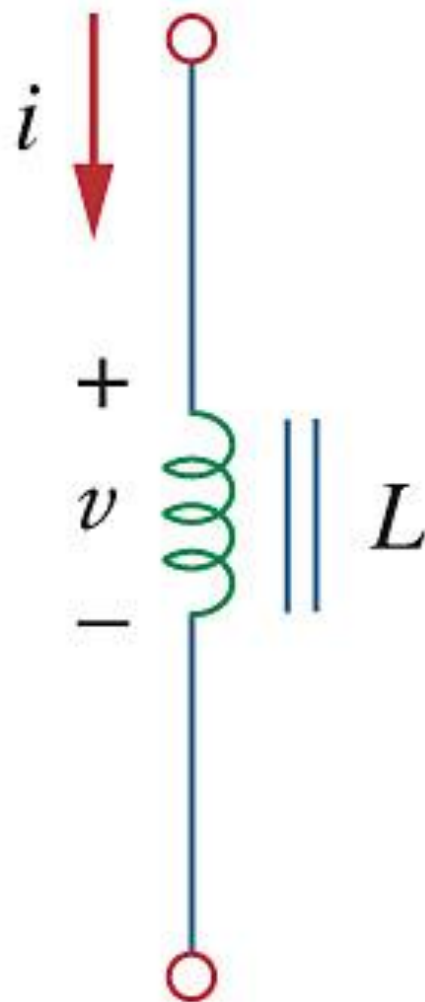


(b)

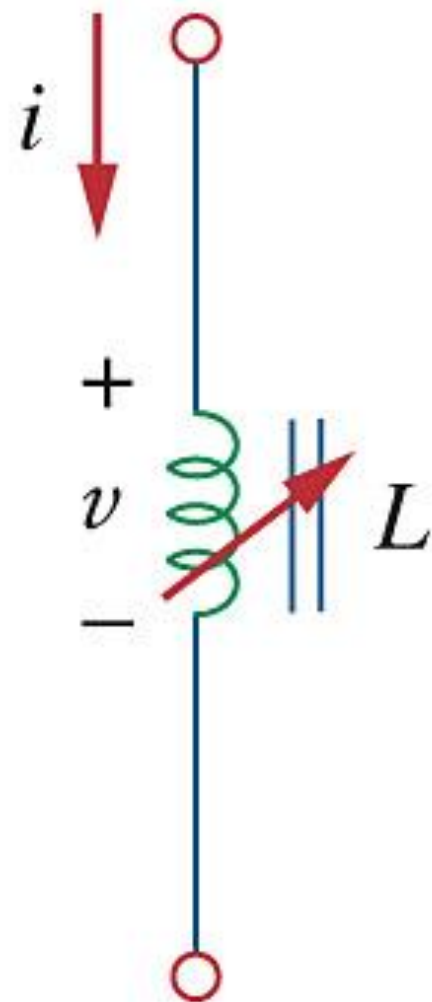

(c)

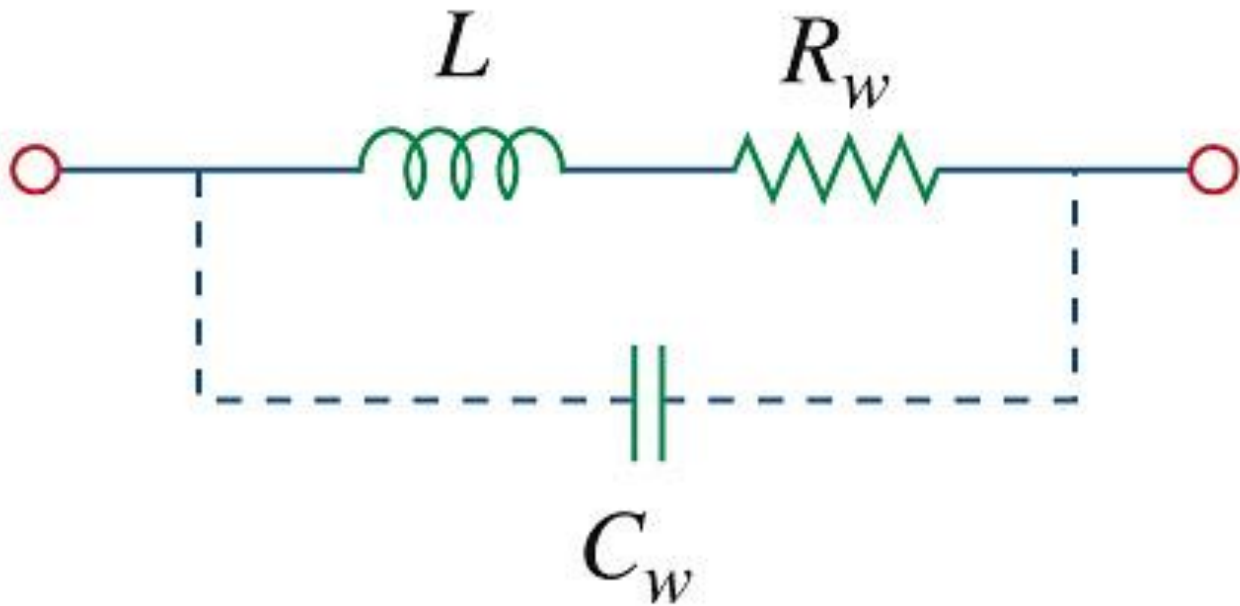Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



## 6.3 Inductors (2)

- Inductance is the property whereby an inductor exhibits opposition to the change of current flowing through it, measured in henrys (H).

$$v = L \frac{d i}{d t}$$

$$L = \frac{N^2 \mu A}{l}$$

- The unit of inductors is Henry (H), mH ( $10^{-3}$ ) and  $\mu\text{H}$  ( $10^{-6}$ ).


## 6.3 Inductors (3)

- The current-voltage relationship of an inductor:

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

- The power stored by an inductor:

$$w = \frac{1}{2} L i^2$$

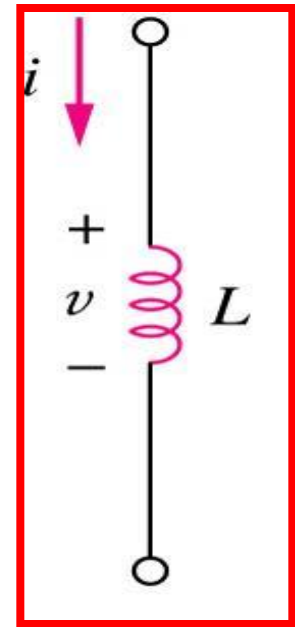

- An inductor acts like a short circuit to dc ( $di/dt = 0$ ) and its current cannot change abruptly.

## 6.3 Inductors (4)

### Example 5

The terminal voltage of a 2-H inductor is

$$v = 10(1-t) \text{ V}$$


Find the current flowing through it at  $t = 4 \text{ s}$  and the energy stored in it within  $0 < t < 4 \text{ s}$ .

Assume  $i(0) = 2 \text{ A}$ .

**Answer:**

$$i(4\text{s}) = -18\text{V}$$


$$w(4\text{s}) = 320\text{J}$$

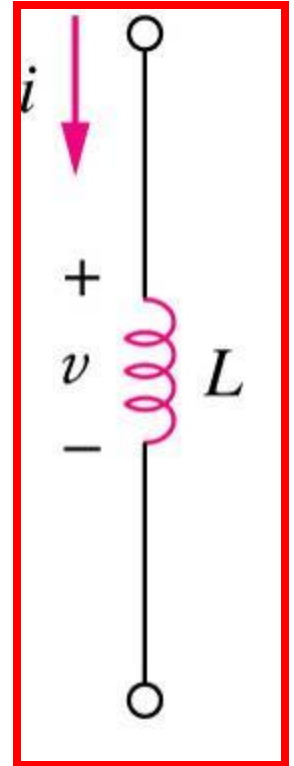

## 6.3 Inductors (5)
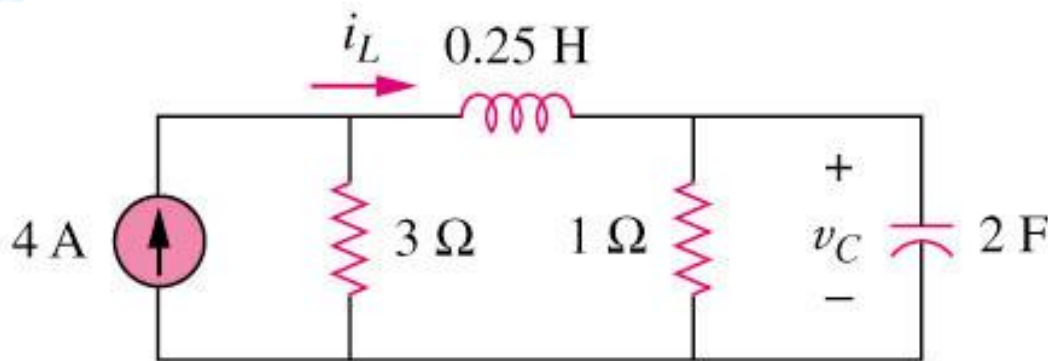
### Example 6

Determine  $v_C$ ,  $i_L$ , and the energy stored in the capacitor and inductor in the circuit of circuit shown below under dc conditions.



**Answer:**

$$i_L = 3A$$


$$v_C = 3V$$

$$w_L = 1.125J$$


$$w_C = 9J$$
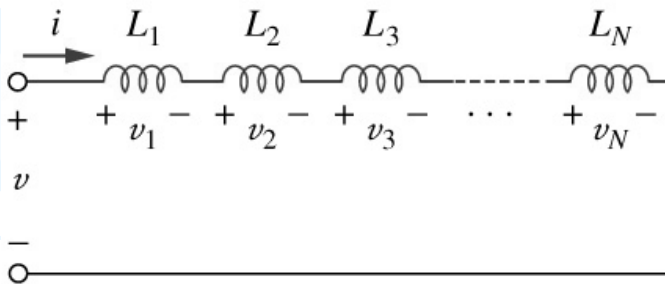
# 6.4 Series and Parallel Inductors (1)

- The equivalent inductance of **series-connected** inductors is the sum of the individual inductances.



(a)

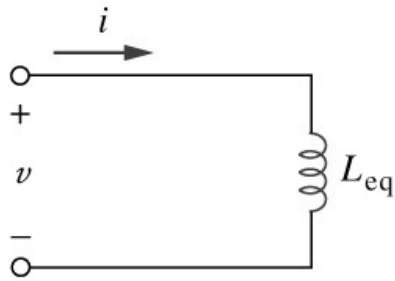


(b)


$$L_{eq} = L_1 + L_2 + \dots + L_N$$
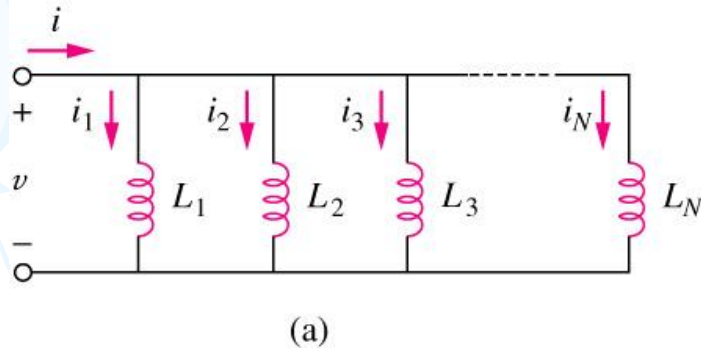
# 6.4 Series and Parallel Inductors (2)

- The equivalent capacitance of **parallel** inductors is the reciprocal of the sum of the reciprocals of the individual inductances.



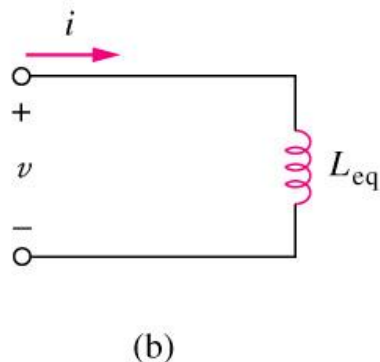
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$



# 6.4 Series and Parallel Inductors (3)
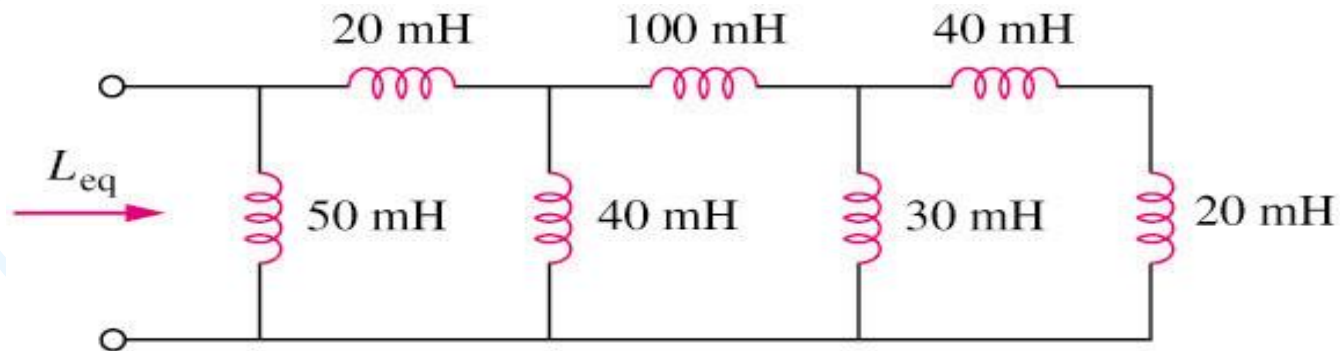
## Example 7

Calculate the equivalent inductance for the inductive ladder network in the circuit shown below:






**Answer:**

$$L_{eq} = \underline{25\text{mH}}$$

# 6.4 Series and Parallel Inductors (4)

- Current and voltage relationship for R, L, C

Circuit element	Units	Voltage	Current	Power
 <p><b>Resistance</b></p>	ohms ( $\Omega$ )	$v = Ri$ <p>(Ohm's law)</p>	$i = \frac{v}{R}$	$p = vi = i^2R$
 <p><b>Inductance</b></p>	henries (H)	$v = L \frac{di}{dt}$	$i = \frac{1}{L} \int v dt + k_1$	$p = vi = Li \frac{di}{dt}$
 <p><b>Capacitance</b></p>	farads (F)	$v = \frac{1}{C} \int i dt + k_2$	$i = C \frac{dv}{dt}$	$p = vi = Cv \frac{dv}{dt}$



# Capacitors and Inductors

## Chapter 6

6.1 Introduction

6.2 Capacitors

6.3 Series and Parallel Capacitors

6.4 Inductors

6.5 Series and Parallel Inductors

6.6 Applications