
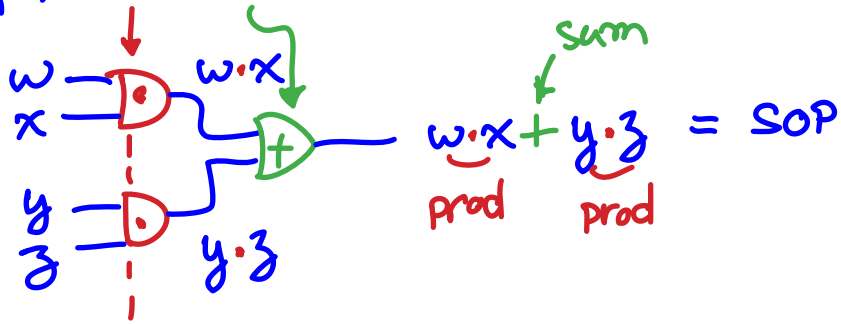


Two-Level Logic Circuits:

1. AND-OR

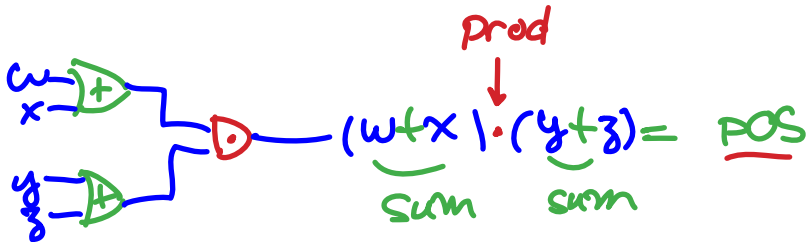

2. OR-AND:



3. XOR-XOR

