
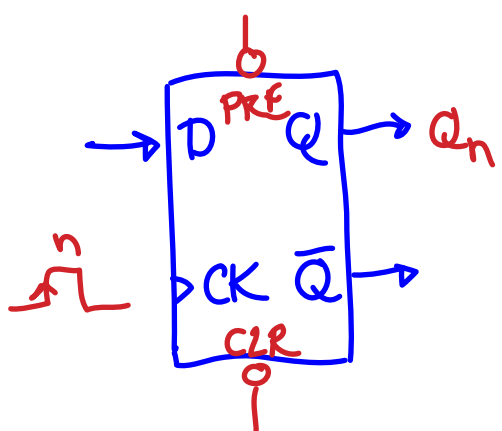


D-flip/flop

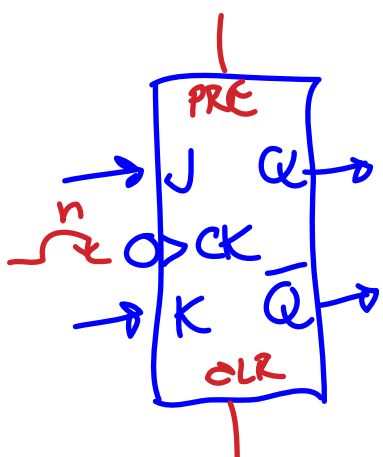

D	NS	Q_{n+1} (rising edge clock)
0	0	Reset
1	1	Set

J-K flip/flop



J	K	NS	Q_{n+1} (falling edge clock)
0	0	Q_n	NC
0	1	0	R
1	0	1	Set
1	1	\bar{Q}_n	Toggle

CLOCK

