

State Any Assumptions You Need To Make – Show All Work – Circle Any Final Answers

Use Your Time Wisely – Work on What You Can – Be Sure to Write Down Equations

Feel Free to Ask Any Questions

☆2a ☆2b ☆2c ☆2e

EXAM 2 [FORM - A] PHYS-207 (KALDON-8)

SPRING 2003

WMU

$$k = 8.988 \times 10^9 \text{ N} \cdot \text{m}^2 / \text{C}^2$$

$$e = 1.602 \times 10^{-19} \text{ C}$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2 / \text{N} \cdot \text{m}^2$$

$$m_e = 9.11 \times 10^{-31} \text{ kg}$$

Don't Panic. Just Follow the Wires and Make the Connections (50,000 points)

1.) (a) You are given two square metal plates with sides $a = 5.00 \text{ cm}$. Design an air filled capacitor, such that when hooked up to a 9.00 volt battery and fully charged, it will spark across the gap and discharge. What is the capacitance C of this badly designed capacitor? *Do not say that the answer is zero... (grin).*

$$\begin{aligned} E_{\max} &= 3,000,000 \text{ V/m} \\ V &= E_{\max} d \\ d &= \frac{V}{E_{\max}} = \frac{9.00 \text{ volts}}{3,000,000 \text{ V/m}} = 0.00000300 \text{ m} \\ C &= \epsilon_0 \frac{A}{d} = (8.85 \times 10^{-12} \text{ C}^2 / \text{N} \cdot \text{m}^2) \frac{(0.0500 \text{ m})^2}{(0.00000300 \text{ m})} \\ &= 7.375 \times 10^{-9} \text{ F} = 7375 \text{ pF} \end{aligned}$$

(b) A brand fresh 6.00 volt battery acts like a perfect battery at time $t = 0$ and delivers a current of 1.63 A. At some later time, as the real battery weakens, the current drops to 1.51 A. Find the internal resistance r of the weak battery.

Perfect Battery



Real Battery = Perfect Battery w/ Internal Resistance

$$\begin{aligned} \mathcal{E} &= i R \\ R &= \frac{\mathcal{E}}{i} = \frac{6.00 \text{ volts}}{1.63 \text{ A}} = 3.681 \Omega \end{aligned}$$

$$\begin{aligned} V &= IR \quad \text{or} \quad \mathcal{E} = I(r + R) \\ \mathcal{E} - Ir &= IR \\ \mathcal{E} &= Ir + IR \\ Ir &= \mathcal{E} - IR \\ r &= \frac{\mathcal{E} - IR}{I} \\ &= \frac{6.00 \text{ volts} - (1.51 \text{ A})(3.681 \Omega)}{1.51 \text{ A}} \\ &= 0.2925 \Omega \end{aligned}$$

(c) A 311 Ω resistor is made of three identical resistors ($R = R_1 = R_2 = R_3$) as shown. Find R.



Same Circuit:

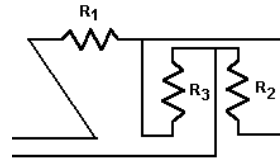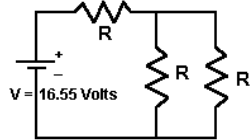

<i>Parallel</i>	<i>Series</i>
$\frac{1}{R_{23}} = \frac{1}{R} + \frac{1}{R} = \frac{2}{R}$	$R_{123} = R + \frac{R}{2} = \frac{3}{2} R = 311 \Omega$
$R = \frac{2(311 \Omega)}{3} = 207.3 \Omega$	

(d) A 311 pF capacitor is made of three identical capacitors ($C = C_1 = C_2 = C_3$) as shown. Find C.

Same Circuit:

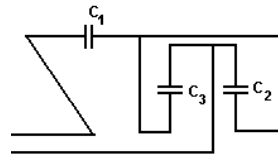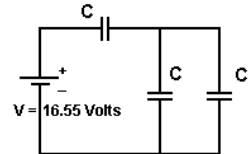

<i>Parallel</i>	<i>Series</i>
$C_{23} = C + C = 2C$	$\frac{1}{C_{123}} = \frac{1}{C} + \frac{1}{2C} = \frac{3}{2C}$
$C_{123} = \frac{2}{3} C$	
$C = \frac{3}{2} C_{123} = \frac{3(311 pF)}{2} = 466.5 pF$	

(e) A particular circuit generates 125 W of Joule heating when hooked up to a perfect battery which has a potential difference of 6.00 volts. If the perfect battery is replaced with another perfect battery of half the voltage, find the power dissipated by Joule heating in this new circuit.

$P = \frac{V^2}{R} \quad ; \quad R = \frac{V^2}{P} = \frac{(6.00 \text{ volts})^2}{125 \text{ W}} = 0.2880 \Omega$
$P = \frac{V_2^2}{R} = \frac{(3.00 \text{ volts})^2}{125 \text{ W}} = 31.25 \text{ W}$

Just A Couple of Easy Star Problems – Nothing to Worry About (50,000 points)

2.) ☆(a) A capacitor C is placed in a circuit where the current leading to the capacitor is given by $I(t) = I_0 \sin(\omega t)$. Find the charge on the capacitor as a function of time, $q(t)$.

$$i = \frac{dq}{dt} ; \quad dq = i dt$$

$$q = \int dq = \int i dt = \int I_0 \sin(\omega t) dt$$

$$q(t) = \frac{-I_0 \cos(\omega t)}{\omega} + C$$

☆(b) An electron enters a velocity selector at its designed speed v . It has velocity $\vec{v} = v \hat{i}$, E-field $\vec{E} = E \hat{j}$ and B-field $\vec{B} = B \hat{k}$. Find the work, $W = \int_a^b \vec{F} \cdot d\vec{s}$, done by the electric force on the electron.

$$W = \int_a^b \vec{F} \cdot d\vec{s}$$

$$d\vec{s} = dx \hat{i}$$

$$\vec{F}_E = -e E \hat{j}$$

$$\vec{F}_E \cdot \hat{i} = 0$$

So...

$$W = 0$$

☆(c) It takes work to store energy in a capacitor as it charges. Integrate $W = \int_0^Q \Delta V dq$ to find this energy.

$$C = \frac{Q}{V} = \frac{Q}{\Delta V} ; \quad \Delta V = \frac{Q}{C} = \frac{q}{C}$$

$$W = \int_0^Q \Delta V dq = \int_0^Q \frac{q}{C} dq$$

$$= \frac{1}{C} \int_0^Q q dq = \frac{1}{C} \left. \frac{q^2}{2} \right|_0^Q = \frac{Q^2}{2C} - 0 = \frac{Q^2}{2C}$$

(d) At the magnetic North Pole, the B-field lines point straight down. An electron ends up going around and around in a horizontal circle of radius $r = 1.00 \text{ cm}$. Find the speed v of the electron.

Given: $B = 1.00 \text{ Gauss} = 1.00 \times 10^{-4} \text{ T}$

$$F_B = F_c$$


$$qvB = ma_c = \frac{mv^2}{r}$$

$$qB = \frac{mv}{r}$$

$$v = \frac{qBr}{m} = \frac{(1.602 \times 10^{-19} \text{ C})(1.00 \times 10^{-4} \text{ T})(0.0100 \text{ m})}{(9.11 \times 10^{-31} \text{ kg})}$$

$$= 175,900 \text{ m/s}$$

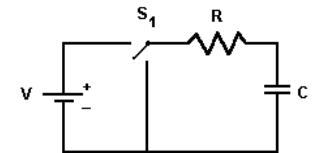☆(e) Consider an RC circuit as shown. Flip the switch S_1 to the left and the capacitor charges. Once charged with a charge $\pm Q_0$, if the switch S_1 is turned down, then the capacitor discharges. For the discharging capacitor, write a Kirchhoff's Law voltage loop equation. Remember that the definition of current is $I = dq/dt$. Show that $Q(t) = Q_0 e^{-t/RC}$.



FOR EITHER CHARGING OR DISCHARGING CAPACITOR, SEE YOUR NOTES...