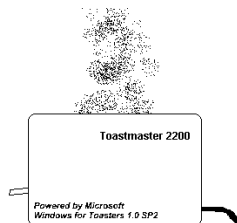


**State Any Assumptions You Need To Make – Show All Work – Circle Any Final Answers**  
**Use Your Time Wisely – Work on What You Can – Be Sure to Write Down Equations**  
**Feel Free to Ask Any Questions**      ☆2a   ☆2b   ☆2c   ☆2e

**“Care For Some Toast?” THE TOASTER IN THE BBC TV SHOW RED DWARF (35,000 pts.)**

1.) (a) A toaster generates Joule heating at a rate of 855 W when plugged into a 125 volt D.C. power source. This results in a current of  $I = 6.84 \text{ A}$ . The nichrome wire used in the heating element is a high resistance wire, but still the entire heating element only has a resistance of  $R = 18.3 \Omega$ . The heating element can be unfolded to be a single coil 0.500 cm in diameter and 45.0 cm long, with 480. turns. Find the inductance,  $L$ , of this coil.


NOTE: If you do not get an answer to (a), use  $L = 252 \text{ mH}$  in parts (b) - (e).



(b) If this toaster into an AC wall outlet, with  $V_{rms} = 125 \text{ volts}$  and  $f = 60.0 \text{ Hz}$ , find the inductive reactance,  $X_L$ , of the heating element.

(c) Sketch a single phasor diagram showing  $v_R$ ,  $v_L$ , and the current,  $i$ .

	"In Use" Equation	"By Geometry" Equation
R	$V = IR$	$R = \frac{\rho L}{A}$
C	$Q = CV$	$C = \epsilon_0 \frac{A}{d}$ (Parallel Plate Capacitor)
L	$L = \frac{N\Phi_B}{I}$	$L = \frac{\mu_0 N^2 A}{l}$ (Air-Core Solenoid)

 


(d) The heater element can be thought of as being a resistor and an inductor in series. What is the time constant of this RL circuit?

(e) Use the impedance to find  $I_{max}$  for the toaster. There is no capacitive nature to this circuit.

**Star Problems in Flight... Afternoon Delight! (30,000 points)**

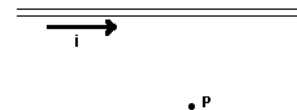2.) ☆(a) A current of 4.35 A flows in a long straight wire. Use Ampere's Law to find  $\vec{B}$  at point  $P$  which is 15.0 cm (0.150 m) directly below the long straight wire. *This is a Star Problem – “Show Me The Integral!”*



☆(b) The differential equation for an ideal LC circuit is  $\frac{d^2Q}{dt^2} = -\frac{1}{LC} Q$ , whose solutions are


mathematically the same as the Simple Harmonic Oscillator in PHYS-205. Create this equation by starting with the knowledge that the change in the total energy stored in both the inductor and the

capacitor is zero,  $\frac{dU}{dt} = \frac{d}{dt} \left( \frac{Q^2}{2C} + \frac{1}{2} LI^2 \right) = 0$  and remembering that  $I = \frac{dQ}{dt}$ .

☆(c) Starting from the equation for an inductor with  $N$  turns,  $L = \frac{N\Phi_B}{I}$ , show that the right-hand equality

of the self-induced emf equation for a coil in a magnetic field  $\mathcal{E}_L = -N \frac{d\Phi_B}{dt} = -L \frac{dI}{dt}$ , is true.

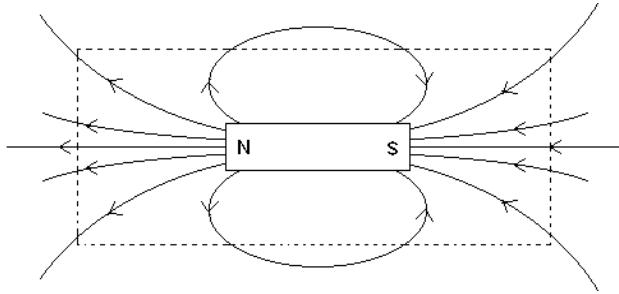
(d) Although we don't want to calculate all the little bits and pieces (we don't really have the equations), consider a permanent magnet inside a Gaussian surface of some symmetric shape. What can you say about the magnetic flux,  $\Phi_B$ , such that Gauss' Law for Magnetism,  $\oint \vec{B} \cdot d\vec{A} = 0$ , holds true?



★(e) A 15 turn coil of cross-sectional area  $0.00785 \text{ m}^2$  and length  $0.0500 \text{ m}$ , experiences a uniform magnetic field directly down its length of magnitude  $B(t) = 5.00T + (5.00T / \text{sec})t - (5.00T / \text{sec}^2)t^2$ . Find the induced current, if any, in the coil at the time  $t = 5.00 \text{ seconds}$ .

**Power to the People! (35,000 points)**

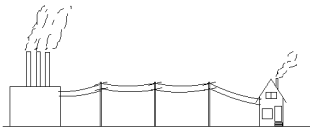3.) (a) Two parallel power lines each carry 480. A of current in the same direction. If the cables between two power poles are 85.0 m long and are separated by a distance of 3.50 meters, find the magnetic force between the two power lines, and indicate whether they are attracted or repelled. *For simplicity's sake, treat this as D.C. in this part, even though we know that the power lines are really A.C.*



(b) At the house of a mad scientist, Dr. Fyl, the 480. A is used at 118 V A.C. to power his cathedral of Micron Millennia Pentium computers. The power plant is 25.0 km away, and 50.0 km of wires (*to and from*) has a total resistance of  $22.5 \Omega$ . If 480. A runs through the wires, find the efficiency of this power distribution system.

(c) If instead, the electricity is set at 118,000 V A.C. on the power lines, find the new efficiency of the power distribution system.

(d) The voltage is changed by a step-down transformer from 118,000 volts to 118 volts. The secondary coil has  $N_2 = 1000$ . turns. How many turns does the primary loop have?

(e) Our transformer is sketched below – note that both sides have the same number of turns so as not to suggest an answer for (d)! If at some time  $t_0$  that the primary current  $I_1$  is increasing and going to the right as shown, then explain whether the induced current of the secondary,  $I_2$ , goes to the LEFT or to the RIGHT.

