

ECE 2100 Circuit Analysis
Fall 2019
Final Exam

NAME: _____

INSTRUCTIONS:

1. **THIS EXAM IS CLOSED BOOK AND CLOSED NOTES.**
A “Potentially Useful Facts” sheet is provided.
2. **NO ELECTRONIC DEVICES ARE ALLOWED.**
All electronic devices, *including watches*, must be stowed away.
3. You may only use the provided pencil.
All other writing instruments and erasers must be stowed away.
4. No hats or hoods may be worn during the exam.
5. Work each problem in the provided space.
6. **Show ALL work** required to arrive at a solution for either full or partial credit.
7. **READ** the entire question before answering.
8. Have your student ID on your desktop for inspection by the instructor.
9. **SIGN** the honesty pledge at the bottom of the page.
Exams without a signature will receive no credit.

I have neither given nor received assistance from anyone in regards to completion of this exam. I have followed the instructions as provided on this sheet.
I HAVE VERIFIED THAT THIS EXAM HAS (9) PAGES.


SIGNATURE: _____ DATE: _____

Note: Schematics prepared using LTspice® (linear.com).

Potentially Useful Facts (updated 4 December 2019)


1. $A \angle \theta = Ae^{j\theta} = A \cos \theta + A \sin \theta j$
2. $v = L \frac{di}{dt}$ (follows passive sign convention)
3. $i = C \frac{dv}{dt}$ (follows passive sign convention)
4. $\vec{Z}_L = j\omega L$
5. $\vec{Z}_C = \frac{1}{j\omega C}$
6. $\vec{S} = \vec{V}_{RMS} (\vec{I}_{RMS})^*$ (follows passive sign convention)

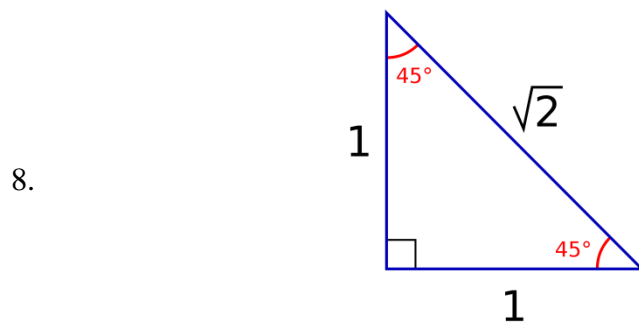7.
$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$



source (released to public domain):
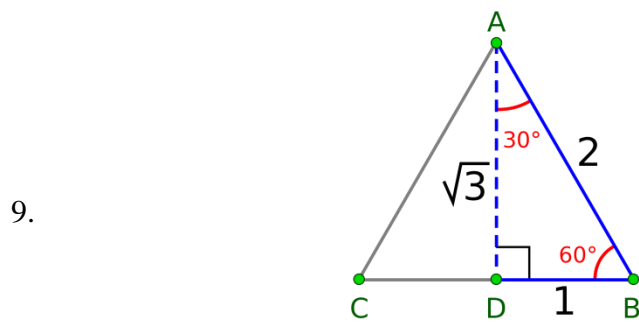
<https://commons.wikimedia.org/wiki/File:45-45-triangle.svg>



source (released to public domain):

<https://commons.wikimedia.org/wiki/File:30-60-90.svg>

10. first-order DC circuit response

$$x(t) = x(\infty) + [x(0) - x(\infty)]e^{-t/\tau}$$

$$\tau = R_{eq}C \text{ or } L/R_{eq}$$

Exam score is out of 32 points; 33 points are possible.

1. (5 points is full credit, 6 points possible)


The op-amps in the circuit on the next page are ideal.

Find the following quantities. **Put answers in table.**


Do not panic!

First find V_b and V_c ; then I_1 ; then V_a and V_d ; then V_+ ; then I_2 ; then V_o .

Power of V_1	
Node voltage V_a	
Node voltage V_d	
Node voltage V_+	
Current I_2	
Node voltage V_o	
quantity	ans.

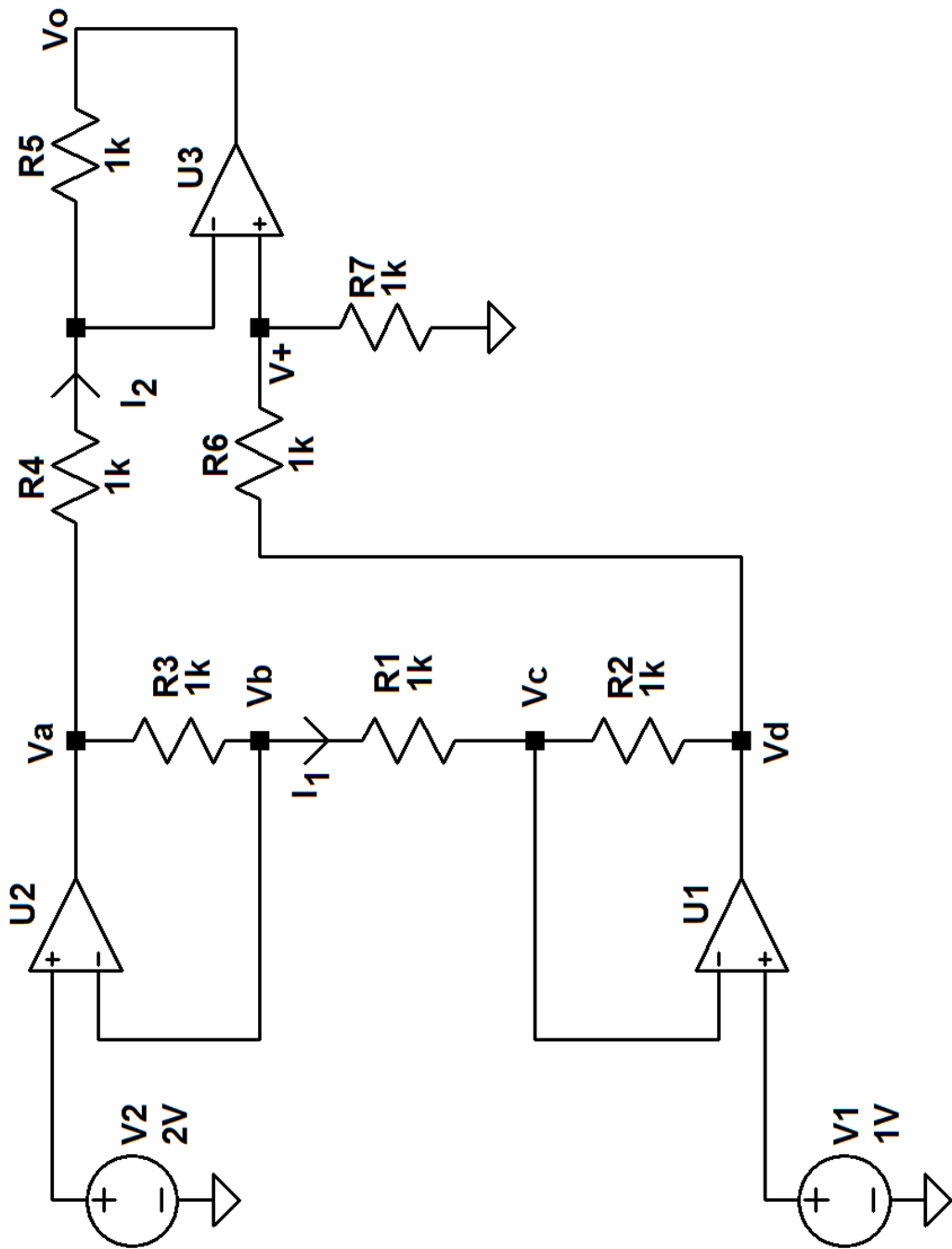

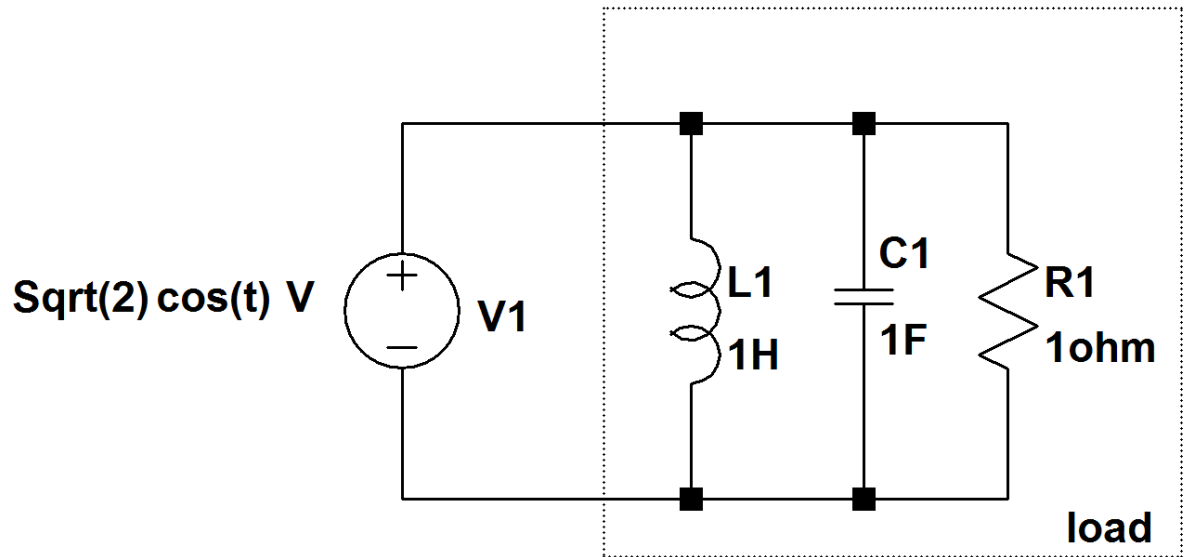2. (5 points) Consider the following circuit.
Find the complex power of the load (consisting of L1, C1, and R1).



THERE ARE TWO PROBLEMS ON THIS PAGE

3. (5 points) The complex power of a load is $\bar{S}=1 - j$ VA. If the load voltage is 10V RMS and the frequency is 10 rad/s, find the value of a component to put in parallel with the load so that the new load has a unity power factor.
Your work must be clear – as always, watch units!

4. (2 points) Consider the system


$$y = T[x] = m x$$

where x is the system input and y is the system output.


Find a non-zero finite value of m so that this system is linear.

Justify your response. No partial credit.

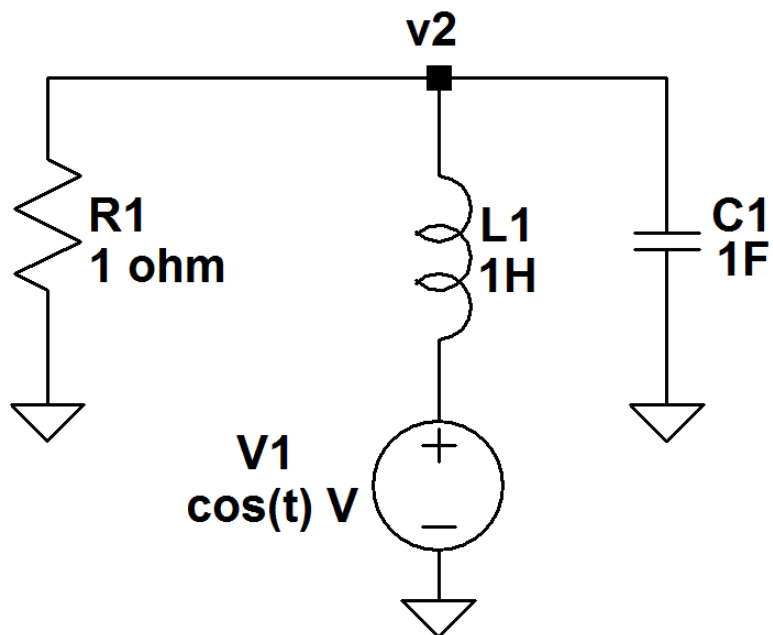5. (5 points) Find node voltage $v_2(t)$ in the sinusoidal steady state using **nodal analysis**.



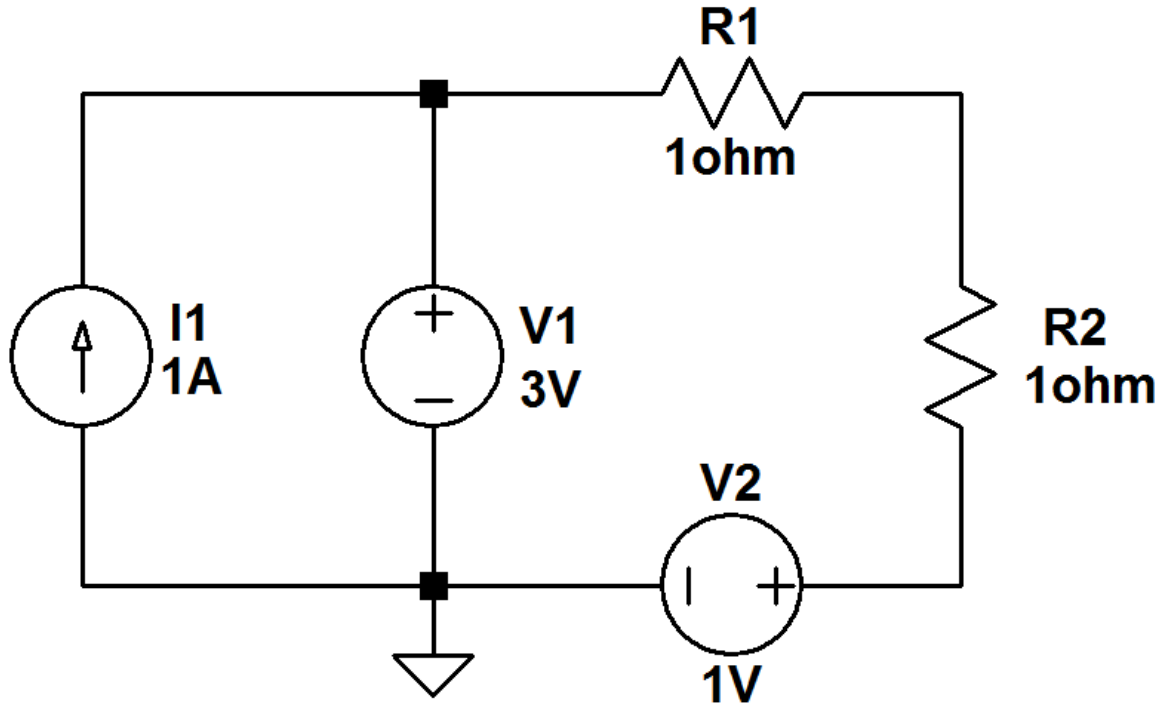6. (5 points) Find the power of each circuit element.
 You **must** show the voltage across (with polarity) and current through (with direction) each element. Put answers in table.



ELEMENT	POWER
I_1	
V_1	
V_2	
R_1	
R_2	

7. (5 points) The switch is OPENED at $t=0$ after being closed for a long time. Find the current $i(t)$ for $t \geq 0$.

