

Nodal and Mesh Analysis: Comparison of Analysis, Simulated, and Experimental Results

ECE 2100 Circuit Analysis
version 30 September 2021

Equipment and Supplies

variable DC voltage source
digital multimeter
resistors (1/4W) 1k Ω ; 2.2k Ω ; 3.3k Ω ; 4.7k Ω ;

Pre-Laboratory Assignment (STEPS 1-8)

1. Consider the circuit of Figure 1. Write nodal analysis equations for node voltages V_2 and V_3 . **Use symbolic voltage source and resistor values, e.g. V_s and R_1 (not 10V and 1k) in your equations.** Note you are given V_1 .
2. Reproduce Table 1 in your lab notebook.
3. Use your equations from pre-lab step 1 to find numeric values for all node voltages and enter into Table 1 analysis column.
4. Consider the circuit of Figure 1. Write mesh analysis equations for mesh currents I_1 and I_2 . **Use symbolic voltage source and resistor values, e.g. V_s and R_1 (not 10V and 1k) in your equations.**
5. Use your equations from pre-lab step 4 to find numeric values for all mesh currents and enter into Table 1 analysis column.
6. Simulate the circuit using LTspice® (DC operating point simulation) and tabulate node voltages and mesh currents in Table 1 simulated column. **Your simulated and analysis results should closely match.**
7. Find the resistance R_{eq} seen by the source; that is, the equivalent resistance between terminals a and b with V_s removed. Enter as R_{eq} in Table I analysis column.
8. Change the LTspice® simulation type to a DC Transfer simulation with Output V(V2) and input V_s . Run the simulation. The input impedance is the equivalent resistance R_{eq} 'seen' by the source. Enter as R_{eq} in simulated column. **Your simulated and analysis result should closely match.**

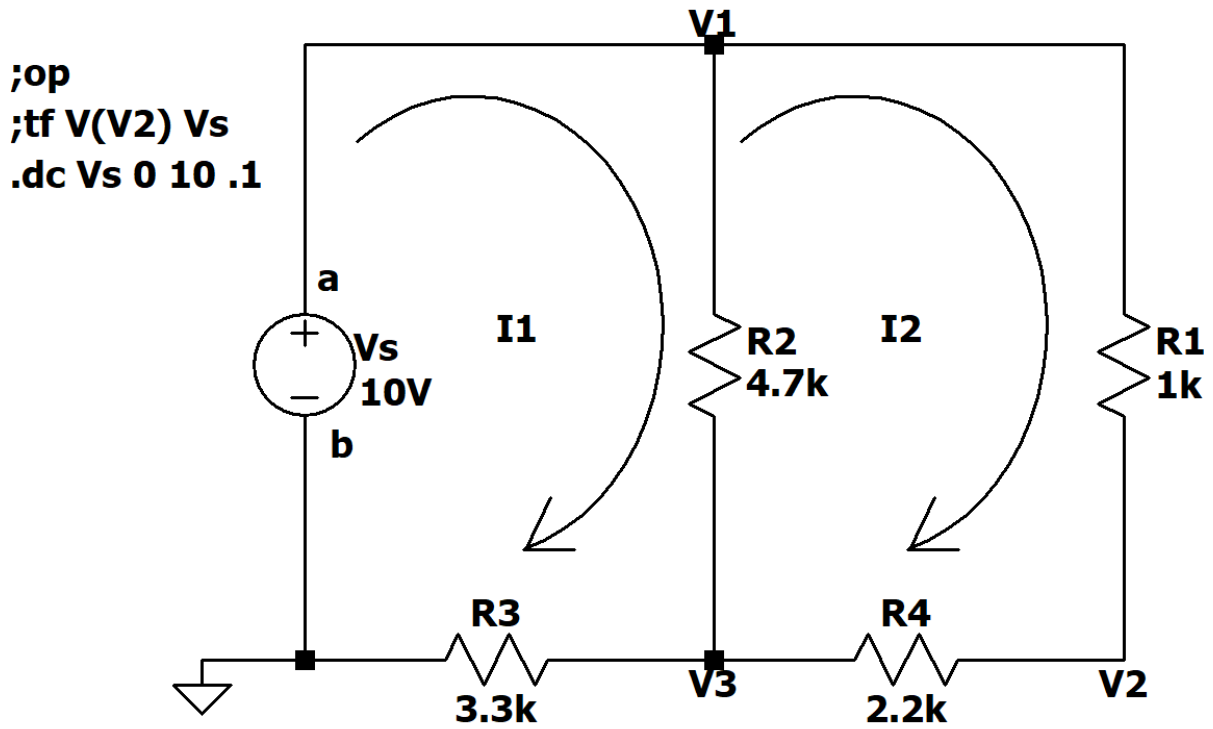


Figure 1. Resistive Circuit

	analysis	simulated	experimental	% error (simulated vs analysis)	% error (experimental vs. analysis)
V _s					
V ₁					
V ₂					
V ₃					
I ₁					
I ₂					
Req					

Table 1. Results

Procedures

Req

1. Construct the circuit of Figure 1 **without the voltage source**.
2. Measure the resistance R_{eq} 'seen' by the voltage source using your ohmmeter. Enter in Table 1 experimental column.

DO NOT PROCEED UNLESS YOUR R_{eq} CLOSELY MATCHES THE PREDICTED VALUE.

Measuring Node Voltages and Mesh Currents

3. Ensure DMM is in voltmeter mode.
Set power supply to 0V.
Set power supply current limit to $1.2 \cdot 10V/R_{eq}$.
Connect the voltage source to the circuit and enable the power supply output.
Starting at 0V slowly adjust the power supply to 10V.

Measure and record the voltage source value V_S in Table 1 experimental column.

4. Measure node voltages and mesh currents. Place your measurements in Table 1 experimental column. Watch units!
5. Power off the circuit.
6. Compute the percentage errors for each row in Table 1 as indicated.
DO NOT DISASSEMBLE YOUR CIRCUIT unless your experimental results match predicted values.

Measuring Resistor Values

7. After circuit disassembly measure and record each resistor value using your ohmmeter. Do not touch resistor ends when measuring resistance. Lay the resistor flat on the bench and then press the probe leads onto the resistor leads while holding only the plastic part of the probes (of course we never touch any part of an energized circuit!).
8. Return DMM to voltmeter mode.

Analysis

1. Why is the current limit set to $1.2 \cdot 10V/R_{eq}$ in lab step 3?
2. Using your equations from the pre-lab and your **measured** resistor and voltage source values, recompute node voltages and mesh currents. Then recompute the experimental errors by comparing experimental values to the updated analysis results. Present your results in a table like Table 1. Did your experimental errors improve?

3. Perform a LTspice® DC Sweep analysis. Use a linear sweep of V_s from 0 to 10V with a 0.1V increment. Plot V_s versus the current provided by V_s . Measure the slope. Compare this value to R_{eq} . Should these numbers match? If your slope is negative, something is wrong (why?).

Credits and Copyright

Adapted from material developed by current and former ECE faculty, including Professor Joseph Kelemen. Thanks to Dr. Binu Narakathu and Brian Durant for improvements to this lab.

© 2021 Damon A. Miller. All rights reserved.