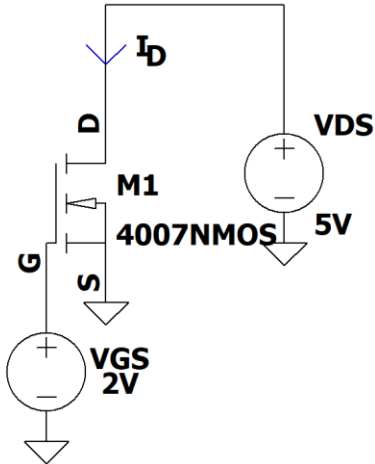


NMOS and PMOS examples using LTspice (linear.com)

© 2020 Damon A. Miller

version 11 March 2020

NMOS




```
.dc VDS 0 5 1mV VGS 0 4 1  
.model 4007NMOS NMOS(LEVEL=2 KP=0.3E-3 VTO=1)
```


SAT CURRENT AT VGS=4 => $KP/2 (4-1)^2 = 1.35\text{mA}$
BODY TO NEGATIVE MOST SUPPLY (0V)

LTspice (linear.com) Basic NMOS Example
(c) 2012 Damon A. Miller

 REF: Sedra and Smith, Microelectronic Circuits, 6th ed.



PMOS

 

```
.dc VDS -5 0 1mV VGS -4 0 1  
.model 4007PMOS PMOS(LEVEL=2 KP=1.0E-3 VTO=-1)  
SAT CURRENT AT VGS=-4V =>  $KP/2 (-4--1)^2 = 4.5\text{mA}$   
BODY TO POSITIVE MOST SUPPLY (0V)
```

LTspice (linear.com) Basic PMOS Example
(c) 2012 Damon A. Miller

REF: Sedra and Smith, Microelectronic Circuits, 6th ed.

